

Basic Electrical Engineering

(BEE)

Unit 1

In which branch , we studies about resistance, inductors, energy sources, electric circuit's elements equipment and components.

Electrical source of energy provides energy to the circuit. These sources are two types -

(i) DC Source

(ii) AC Source

(i) DC Source :-

DC circuits are the circuits which are excited by unidirectional (Direct current) energy source such as batteries, cells etc.

(ii) AC Source :-

AC circuits are the circuits which are excited by alternating current (AC) energy source.

In DC Source , Capacitor and inductor don't show their presence.

• Electric Current :- Current is basically flow of electric charge with respect to time.

$$I = \frac{dQ}{dt}$$
 where Q is charge in coulomb
t is time in seconds


Current is generally measured in Ampere.

Direction of current is the same as the direction of flow of Positive charge which is opposite to the flow of electrons.

There are two types of current-

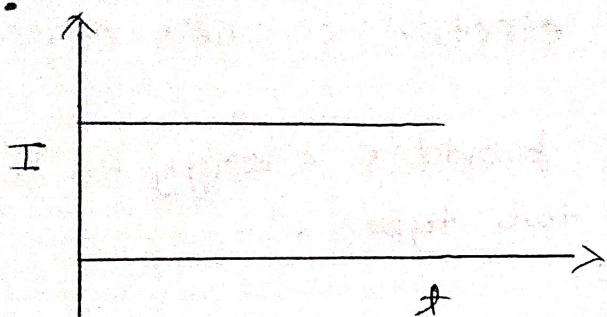
(i) DC Current

- The flow of charge is constant and is in one direction



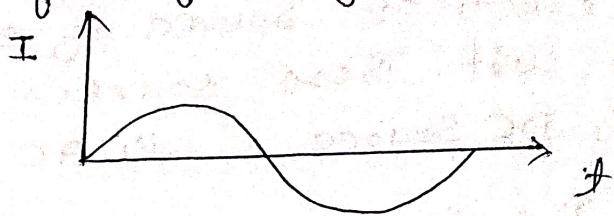(ii) AC Current

- Flow of charge is not uniform. It changes with time.
- Charge flow in one direction for certain time and then flow of charge in other direction



* Electric potential :-

The electric potential of a point may be defined as amount of work done to bring a unit positive charge from infinity to that point.

$$V = \frac{W}{Q}$$



when $Q = 1$ coulomb

$$[V = W/J]$$

The unit of Potential is volt (V)

It is defined for always two points not for singal.

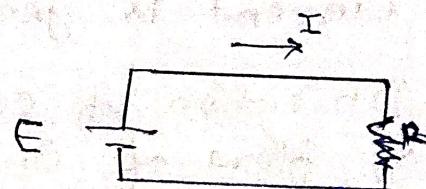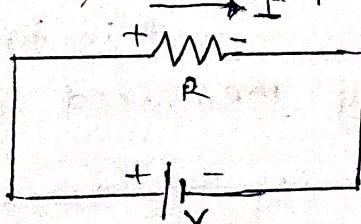higher potential point is termed as positive terminal and the lower potential point is termed as negative terminal.



* Electromotive Force (EMF) :-

Electromotive force is nothing but a voltage generated by a source, such as battery, generator, cell etc. Thus electromotive force (emf) is not a force but a potential which drives the flow of electric current in a circuit.

* Electric Power :-

In an electrical circuit, when flow of charges takes places, some amount of work is done.

The electrical power (P) is defined as amount of work done per unit time.

$$P = \frac{W}{t} = \frac{VQ}{t} = VI$$

Unit of Power is watt (W)

* (1 H.P. = 746 W)

* Ohm's Law :- The current (I) passing through a conductor is directly proportional to the potential difference (V) across the ends of the conductor provided the physical conditions (temperature, resistivity, dimensions etc.) remain the same."

$$I \propto V$$

$$I = \frac{V}{R}$$

Where R = resistance which is measured in ohms.

Resistance :- Resistance is the property of resistor (conductor) which oppose the flow of current.

$$R = \frac{\rho l}{A}$$

l = length of conductor.

A = cross-sectional area

ρ = resistivity of conductor.

$$\Rightarrow G = \frac{1}{R} = \text{Conductance.}$$

[Unit mho = Ω^{-1}]
siemens

\Rightarrow * Reciprocal of ρ is called conductivity.

$$\sigma = \frac{1}{\rho}$$


unit of σ is siemens per meter.

by ohm's law


$$V = IR$$

$$\therefore P = VI$$

$$P = I^2 R = V^2 / R$$

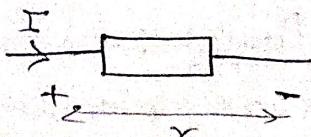

$P = VI$
{ absorbed
consumed}

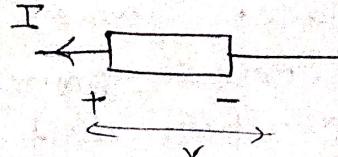

$P = VI$
(delivered)

* Basic elements

Active element

An energy source is said to be an active element of the circuit.

Ex. batteries, generators, properly biased transistors.

~~Kirchhoff's Laws~~


Energy Sources:-

These sources provide necessary excitation to an electric network.


Ideal Sources

- Voltage supply constant
- internal resistance = 0
- independent on others
- efficiency = 100%

Symbols

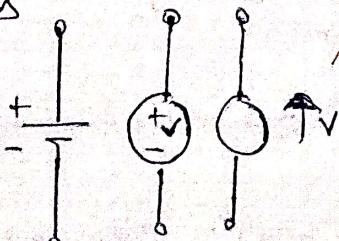


for Ideal current source

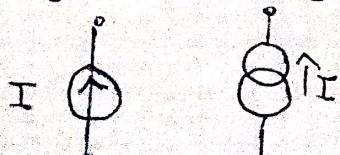


Practical Sources

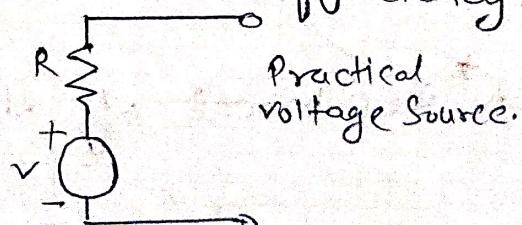- have losses.
- internal resistance ≠ 0
- dependent on others.
- not have ~~100%~~ efficiency.



Practical
voltage Source.

for practical current source

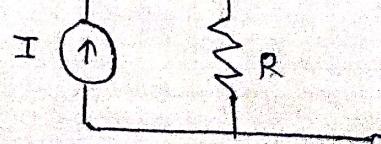


Note

- 1. In Parallel branches, we can't apply different magnitudes.
 - 2. Current can't be connected in series combination.


Source Conversion:-

A practical voltage source can be converted in practical current source and a practical current source can be converted in practical voltage source.

Voltage to Current

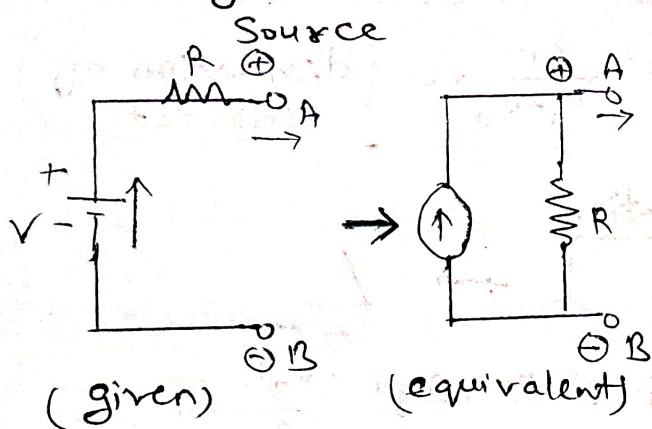


Current to Voltage Source

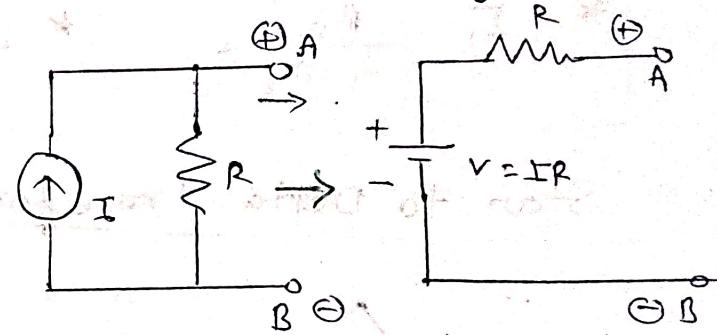

Note The polarity of the terminal should not be changed.

• Resistors in series combination :-

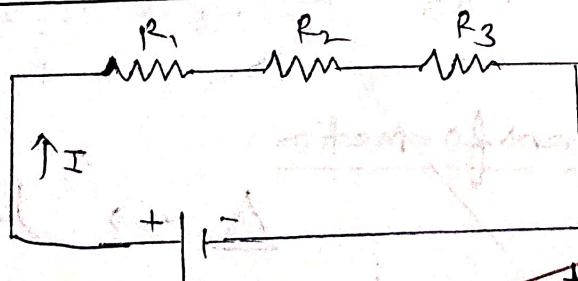

~~Current will flow same
in all resistors in
series comb.~~

$$V_1 = IR_1 \quad V_3 = IR_3$$


$$V_2 = IR_2$$

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

* note

$$V_n = \frac{R_n}{\sum R} \cdot V \quad (\text{deviation of voltage in series})$$

Resistors in Parallel

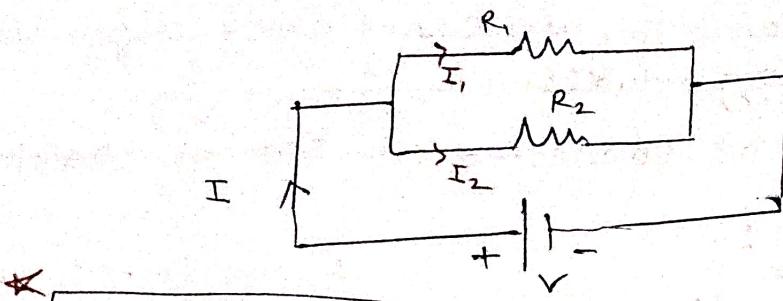

→ they are connected end to end with each other making their ends at common potential.

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


$$\left(\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n} \right)$$

$$(G_{eq} = G_1 + G_2 + G_3 + \dots + G_n)$$

$$I_1 = \frac{R_2}{R_1 + R_2} \times I$$

$$I_2 = \frac{R_1}{R_1 + R_2} \times I \quad (\text{deviation of current})$$

Star to Delta transformation


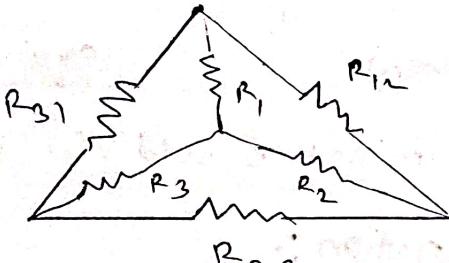


$$R_{31} (= R_1 + R_3 + \frac{R_2 R_1}{R_2})$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

Delta to Star transformation

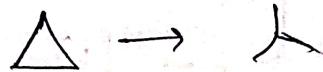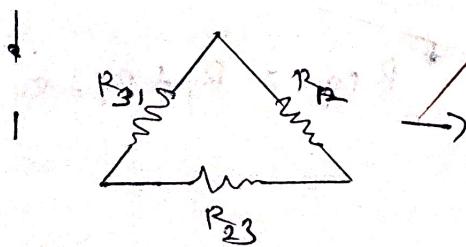

$$R_{12} = \frac{R_{12} R_{23}}{R_1 + R_2 + R_3}$$

$$R_{23} = \frac{R_2 \cdot R_3}{R_1 + R_2 + R_3}$$

$$R_{31} = \frac{R_3 \cdot R_1}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{23} \cdot R_{21}}{R_{12} + R_{23} + R_{31}}$$


$$R_3 = \frac{R_{31} \cdot R_{23}}{R_{12} + R_{23} + R_{31}}$$

* Kirchhoff's Laws :-

There are two types of Kirchhoff's law.

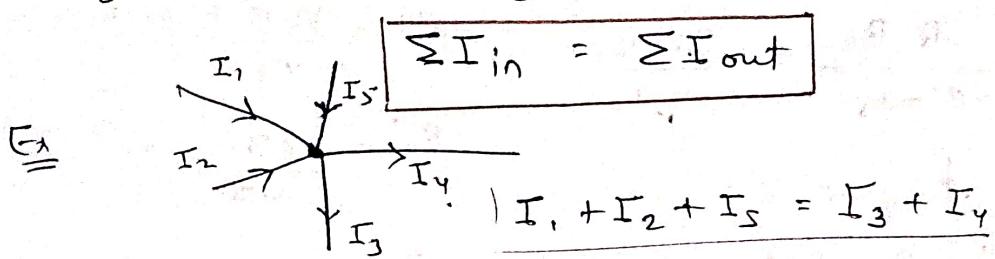1. Kirchhoff's Current Law (KCL) :-

In any electric circuit,
the algebraic sum of all the currents meeting at
any node is zero, $\sum I_{\text{out}} = 0$
or at any node incoming current = sum of outgoing
current



→ This law is based on law of conservation of charges.


2. Kirchhoff's Voltage Law (KVL) :-

In any electrical circuit,

"the algebraic sum of voltage rises is equal to algebraic sum of voltage drops around any closed path (or loop or current)"

$$\sum V_{\text{drop}} = 0$$

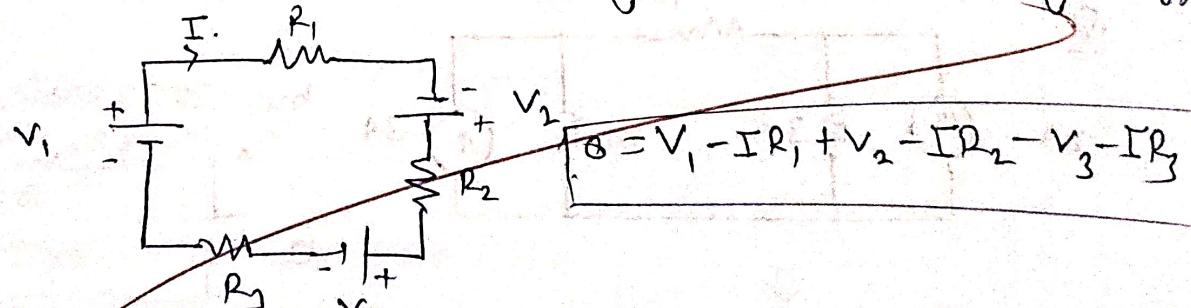→ This law is based on law of conservation of energy.



Note

direction of movement


$$V = -IR$$

otherwise


$$V = IR$$

is
Direction of movement

$$V = +E$$

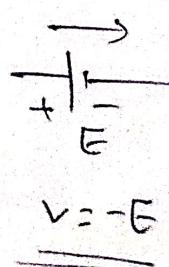

Ex

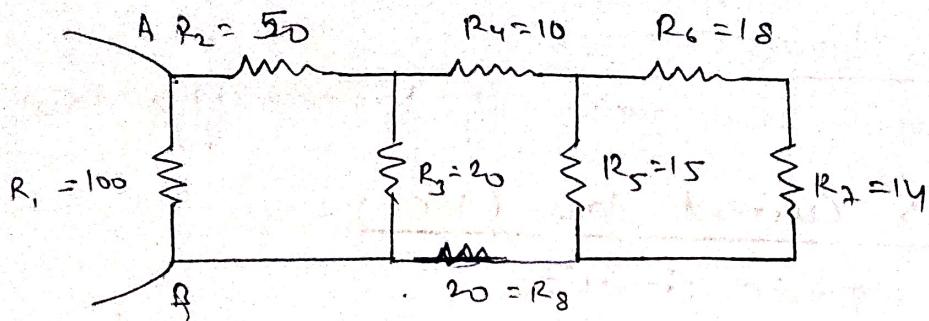

Find resistance between A & B Point

Series ①

$$R' = R_6 + R_7 = 32 \Omega$$

②

$$R'' = R'' + R_8 + R_4 \quad (\text{series})$$

Parallel ②

$$R'' = \frac{R' R_5}{R' + R_5} = \frac{32 \times 15}{47}$$

$$R''' = \frac{32 \times 15 + 20 + 10}{47}$$

$$R''' = \frac{1890}{47} \Omega$$

.f

④

R_3 & R''' = Parallel

⑤ R_2 & R_1 Series

$$R^* = \frac{R_3 R'''}{R_3 + R'''} = \frac{\cancel{1890} * 20}{\cancel{47}} / \frac{\cancel{1890} + 20}{\cancel{47}}$$

$$R^{**} = \frac{3780}{283} + 50 = \frac{27930}{283}$$

$$R^{**} = \frac{3780}{283}$$

now


~~$R^* \parallel R_1$~~ R_1 = parallel

$$R_{eq} = \frac{27930 \times 100}{283}$$



$$\frac{27930 + 28300}{283}$$

$$R_{eq} = 49.67 \Omega \text{ Ans}$$

Q

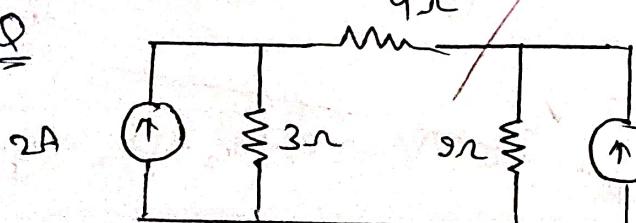



by converting it

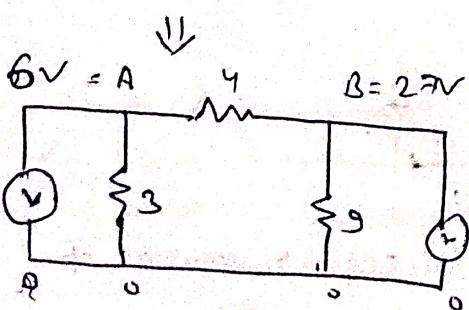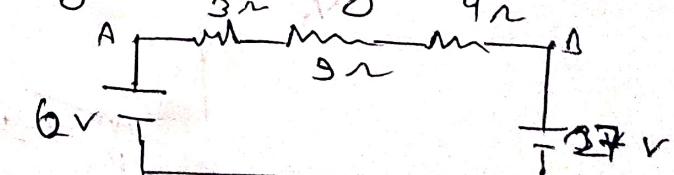

$$V_{tot} = 33V$$

$$I = \frac{33}{R_{eq}} = \frac{33}{3+4+9}$$

$$= 2.1 \text{ Amp}$$

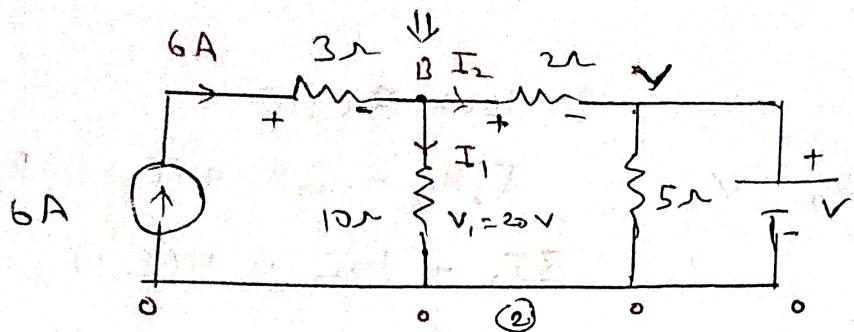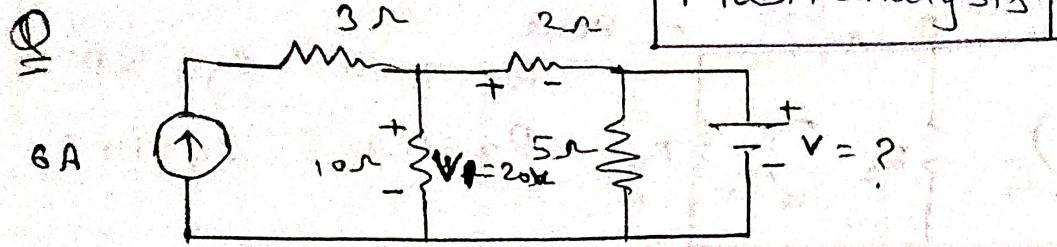

At node B $B = 20V$

$$I_1 + I_2 = 6$$

$$6 = \frac{-v+20}{2} + \frac{-0+20}{10}$$

$$12 = -v+20+4$$

$$B = -v+20$$

$$v = +12V$$

in loop 2
or $-2I_2 - V_{BC} + 20 = 0$

$$-8 - V_{BC} = -20$$


$$(V_{BC} = 12V)$$

$$I_1 + I_2 = 6$$

$$I_2 = 6 - 2$$

$$I_2 = 4 \text{ Amp}$$

Soln

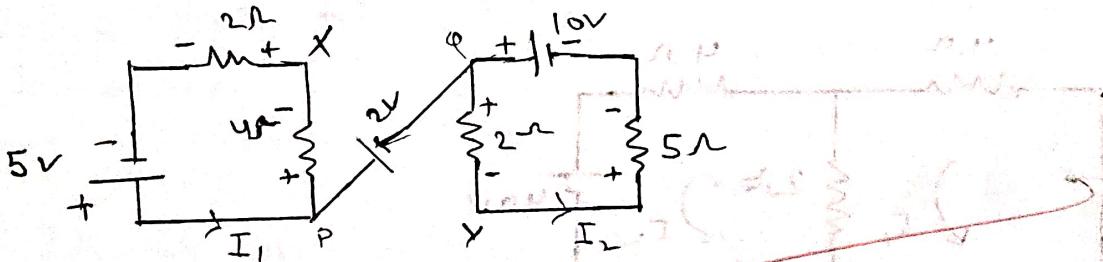

$$V_{xy} = ?$$

Soln

in loop 1

$$I_1 = \frac{5}{6} \text{ Amp}$$

in loop 2

$$I_2 = \frac{10}{7} \text{ Amp}$$

at x, no Hage

$$x - 5 = \frac{5}{6} x$$


at y, voltage

$$V_{xy} = \frac{4 \times 5}{6} - 2 - 2 \times \frac{10}{7}$$

$$x =$$

$$V_{xy} = \frac{10}{3} - 2 - \frac{20}{7} = \frac{70 - 42 - 60}{21}$$
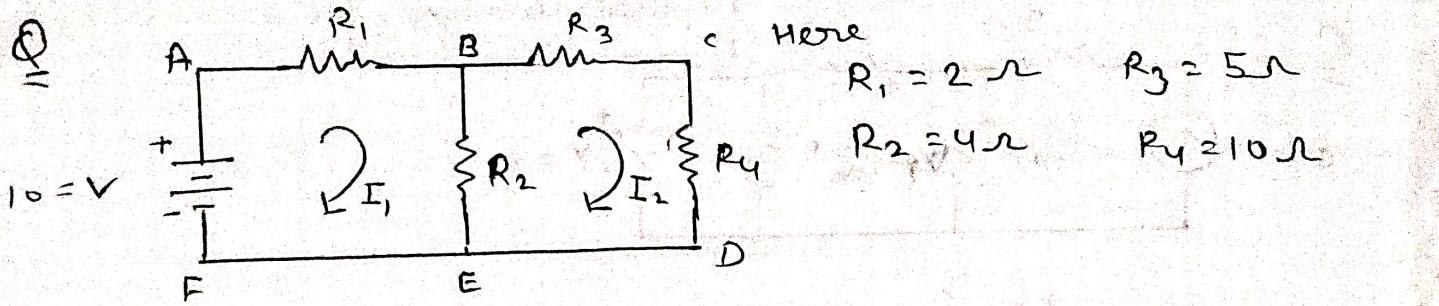
$$V_{xy} = -\frac{32}{21} = 1.51 \text{ Volt}$$



Soln in loop ABFE

$$I_1 R_1 + (I_1 - I_2) R_2 = V \quad \text{in loop BCDE}$$

$$2I_1 + (I_1 - I_2) 4 = 10 \quad I_2 R_3 + I_2 R_4 + (I_2 - I_1) R_2 = 0$$

$$6I_1 - 4I_2 = 10 \quad 5I_2 + 10I_2 + 4(I_2 - I_1) = 0 \quad \text{by (i)}$$


$$\frac{6 \times 19I_2}{4I_2} - 4I_2 = 10 \quad 19I_2 - 4I_1 = 0$$

$$57I_2 - 8I_2 = 20 \quad I_1 = \frac{19I_2}{4}$$

$$49I_2 = 20 \quad I_1 = 0.408 \times 19$$

$$I_2 = \frac{20}{49} \text{ Amp} \quad I_1 = 1.23 \text{ Amp}$$

$I_2 = 0.408 \text{ Amp}$

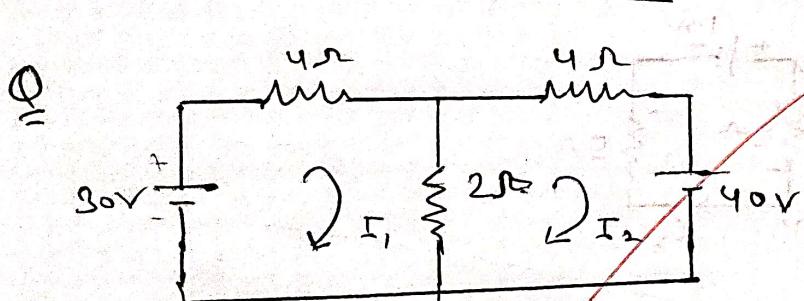

Soln in loop 1

$$4I_1 + 2(I_1 - I_2) = 30 \quad \text{in loop 2}$$

$$4I_2 + (I_2 - I_1) 2 = -40$$

$$6I_2 - 2I_1 = -40$$

$$3I_1 - I_2 = 15 \quad 3I_2 - I_1 = -20 \quad \text{by eq (i) & (ii)}$$


$$3I_1 - I_2 = 15 \quad I_1 = +3 \times 45 - 20$$

$$-3I_1 + 9I_2 = -60 \quad I_1 = +28.125 - 20$$

$$8I_2 = -45 \quad I_1 = 8.125 \text{ Amp}$$

$$I_2 = +5.265 \text{ Amp}$$

Q

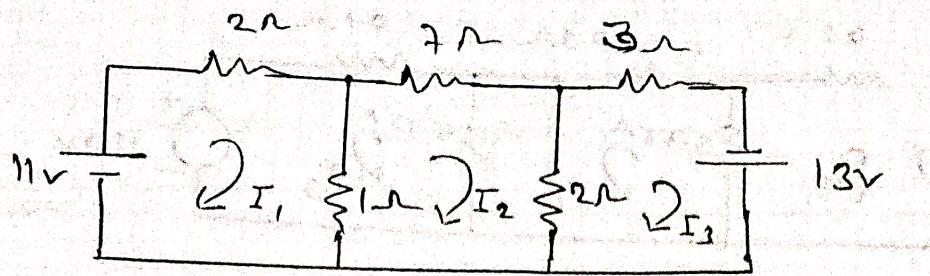

Soln

= in loop 1

in loop 2

$$2I_1 + 1(I_1 - I_2) = 11$$

$$7I_2 + (I_2 - I_3)2 + (I_2 - I_1)1 = 0$$

$$3I_1 - I_2 = 11 \quad \text{(i)}$$

$$10I_2 - 2I_3 - I_1 = 0$$

$$I_1 = 10I_2 - 2I_3 \quad \text{(ii)}$$

in loop 3

by eq (i)

$$3I_3 + (I_3 - I_2)2 = 13$$

$$30I_2 - 6I_3 - I_2 = 11$$

$$5I_3 - 2I_2 = 13 \quad \text{(iii)}$$

$$29I_2 - 6I_3 = 11 \quad \text{(iv)}$$

by eq (ii) & (iii)

$$\begin{array}{r}
 6(5I_3 - 2I_2 = 13) \\
 + 5(-6I_3 + 29I_2 = 11) \\
 \hline
 30I_3 - 12I_2 = 78 \\
 -30I_3 + 145I_2 = 55 \\
 \hline
 133I_2 = 133
 \end{array}$$

$$I_2 = 1 \text{ Amp}$$

by eq (ii)

$$5I_3 - 2(1) = 13$$

$$5I_3 = 15$$


$$I_3 = 3 \text{ Amp}$$

by eq (i)

$$3I_1 - 1 = 11$$

$$I_1 = 1\frac{2}{3}$$

$$I_1 = 4 \text{ Amp}$$

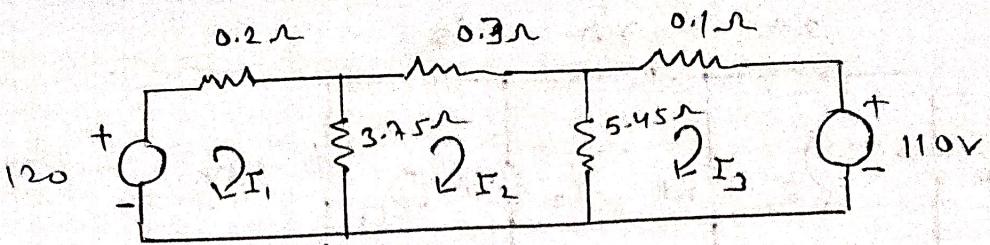

Soln

in loop 1

$$0.2I_1 + (I_1 - I_2)3.75 = 120$$

$$3.95I_1 - 3.75I_2 = 120 \quad \text{---(i)}$$

in loop 2

$$0.3I_2 + (I_2 - I_3)5.45 + (I_2 - I_1)3.75 = 0$$

$$9.5I_2 - 5.45I_3 - 3.75I_1 = 0 \quad \text{---(ii)}$$

$$I_1 = \frac{9.5I_2 - 5.45I_3}{3.75}$$

in loop 3

$$0.1I_3 + (I_3 - I_2)5.45 = -110$$

$$5.55I_3 - 5.45I_2 = -110 \quad \text{---(iii)}$$

by eq (ii) & (iii)

~~$$5.55I_3 - 5.45I_2$$~~

~~$$3.95I_1 - 3.75I_2 = 120$$~~

by eq (iii) & (v)

~~$$3.95[2.53I_2 - 1.45I_3] - 3.75I_2 = 120$$~~

~~$$9.9I_2 - 5.72I_3 - 3.75I_2 = 120$$~~

~~$$6.15I_2 - 5.72I_3 = 120 \quad \text{---(v)}$$~~

by solving them


$$I_1 = 30 \text{ Amp}$$

$$I_2 = 20 \text{ Amp}$$

$$I_3 = 10 \text{ Amp}$$

Nodal Analysis

\therefore

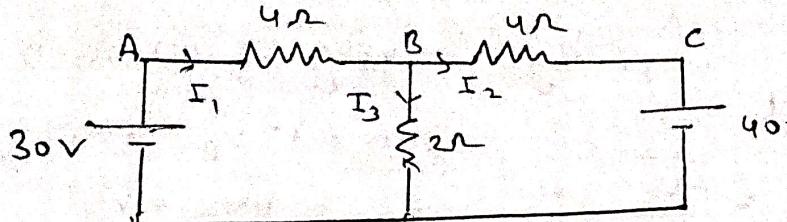

Solve it with nodal method.

$$I_1, I_2 \text{ & } I_3 = ?$$

$$V_A, V_B \text{ & } V_C = ?$$

on node A

$$I_1 = \frac{V_B - V_A}{4}$$

$$I_2 = \frac{V_B - V_C}{4}$$

$$I_3 = \frac{0 - V_B}{2}$$

on node B

$$\frac{V_B - V_A}{4} + \frac{V_B - V_C}{4} = \frac{0 - V_B}{2}$$

$$\frac{V_B - 30}{2} + \frac{V_B - 40}{2} = -V_B$$

$$4V_B = 70$$

$$\boxed{V_B = 17.5 \text{ Volts}}$$

$$I_1 = \frac{17.5 - 30}{4}$$

$$I_1 = 3.125 \text{ Amp}$$


$$I_2 = \frac{17.5 - 40}{2}$$

$$I_2 = 5.25 \text{ Amp}$$

$$I_3 = -\frac{17.5}{2}$$

$$I_3 = -8.39 \text{ Amp}$$

\therefore

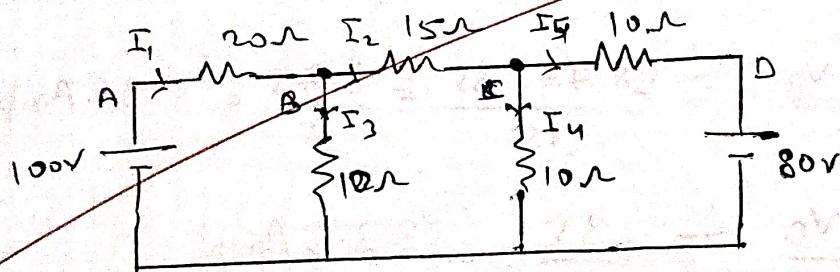

$$I_1 = \frac{V_B - V_A}{20}$$

$$I_2 = \frac{V_C - V_B}{15}$$

$$I_3 = \frac{0 - V_B}{10}$$

$$I_4 = \frac{0 - V_C}{10}$$

$$I_5 = \frac{V_C - V_D}{10}$$

at node B

$$I_1 = I_2 + I_3$$

$$\frac{V_B - 100}{20} = \frac{V_C - V_B}{15} - \frac{V_B}{10}$$

$$\frac{V_B - 100}{4} = \frac{V_C - V_B}{3} - \frac{V_B}{2} \Rightarrow 6V_B - 600 = 20V_B - 8V_C$$

$$300 = 13V_B - 4V_C \quad \text{---(i)}$$

at node c

by Solving eq (i) & (ii)

$$I_2 + I_5 = I_4$$

$$300 = 13V_B - 4V_C$$

$$\frac{V_C - V_B}{15} + \frac{V_C - 80}{10} = \frac{-V_C}{10} + \frac{120}{12} = 4V_C - V_B$$

$$420 = 12V_B$$

$$5V_C - 2V_B - 240 = -3V_C$$

$$240 = 8V_C - 2V_B$$

$$4V_C - V_B = 120 \quad \text{---(ii)}$$

$$V_B = \frac{420}{12} = \frac{70}{2}$$

$$V_B = 35 \text{ Volt}$$

in eq (ii)

$$420 + 35 = 4V_C$$

$$V_C = \frac{455}{4} = 113.75$$

$$\boxed{V_C = 38.75 \text{ volt}}$$


~~$$\text{Now } I_1 = \frac{V_B - V_A}{20} = \frac{35 - 100}{20} = -3.75 \text{ Amp}$$~~

~~$$I_2 = \frac{V_C - V_B}{15} = \frac{38.75 - 35}{15} = \frac{3.75}{15} = 0.25 \text{ Amp}$$~~

~~$$I_3 = \frac{0 - V_B}{10} = \frac{-35}{10} = -3.5 \text{ Amp}$$~~

~~$$I_4 = \frac{0 - V_C}{10} = \frac{-38.75}{10} = -3.875 \text{ Amp}$$~~

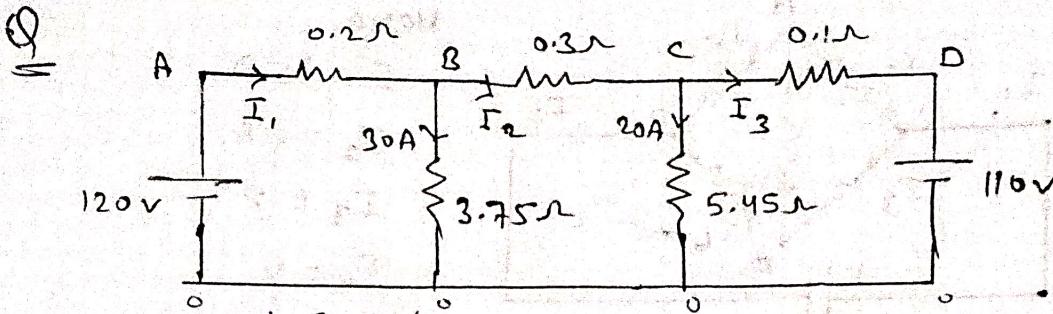~~$$I_5 = \frac{V_C - V_B}{10} = \frac{38.75 - 35}{10} = +0.375 \text{ Amp}$$~~



Solⁿ

$$I_1 = I_2 + 30$$

$$I_2 = 20 + I_3$$

$$I_1 = \frac{V_B - 120}{0.2}$$

$$I_2 = \frac{V_C - V_B}{0.3}$$

$$I_3 = \frac{110 - V_C}{0.1}$$

$$30A = \frac{V_B - V_C}{3.75}$$

$$V_B = -12.5V$$

$$20A = \frac{0 - V_C}{5.45}$$

$$V_C = -109.0V$$

$$\text{in } I_3 = \frac{110 - 109}{0.1} = \frac{1}{0.1}$$

$$\boxed{I_3 = 10 \text{ Amp.}}$$

$$I_2 = 20 + I_3$$

$$\Rightarrow \boxed{I_2 = 30 \text{ Amp}}$$

~~$$I_1 = 30 + 30$$~~

~~$$\boxed{I_1 = 60 \text{ Amp}}$$~~

* Super Node Condition \Rightarrow

when ideal voltage source present b/w two reference node.

procedure \rightarrow

Replace v.s. with their internal γ to apply KCL.


$$V_1 \xrightarrow{R} V_2 \Rightarrow I = \frac{V_1 - V_2}{R}$$

$$V_1 \xrightarrow{R} V_2 \Rightarrow I = \frac{V_1}{R}$$

$$V_1 \xrightarrow{R} E \xrightarrow{V_2} \Rightarrow I = \frac{V_1 - V_2 - E}{R}$$

$$V_1 \xrightarrow{R} V_2 \Rightarrow I = \text{Undifined} \\ (V_1 = V_2)$$

Q1

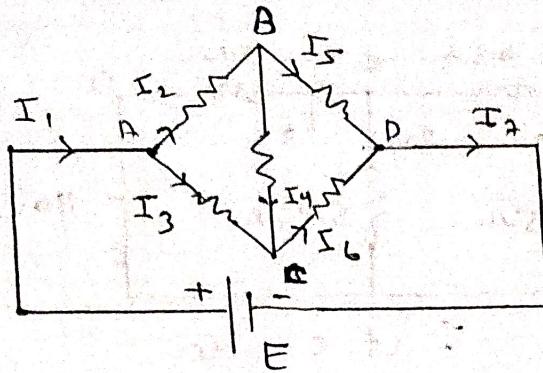

Hence

$$I_1 = 15 \text{ A}$$

$$I_2 = 8 \text{ A}$$

$$I_3 = ?$$

$$I_4 = ?$$

$$I_5 = 6 \text{ A}$$

$$I_6 = ?$$

evaluate unknown current.. $I_6 = ?$

at node A

$$I_1 = I_2 + I_3$$

$$15 = 8 + I_3$$

$$I_3 = 7 \text{ Amp}$$

at node B

$$I_2 = I_4 + I_5$$

$$8 = I_4 + 6$$

$$I_4 = 2 \text{ Amp}$$

at node D

$$I_5 + I_6 = I_7$$

$$6 + 9 = I_7$$


$$I_7 = 15 \text{ Amp}$$

at node C

$$I_3 + I_4 = I_6$$


$$7 + 2 = I_6$$

$$I_6 = 9 \text{ Amp}$$

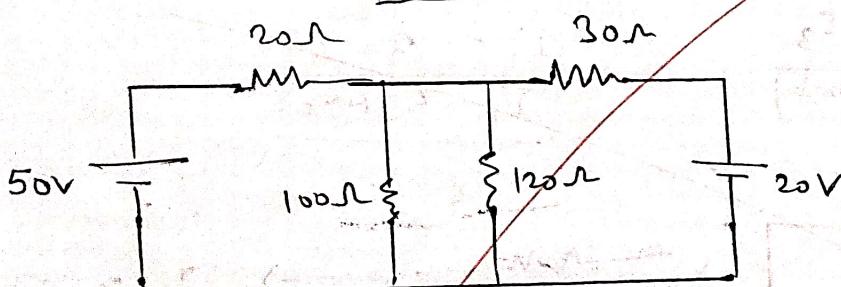

Find current in
100Ω by nodal
method.

Soln

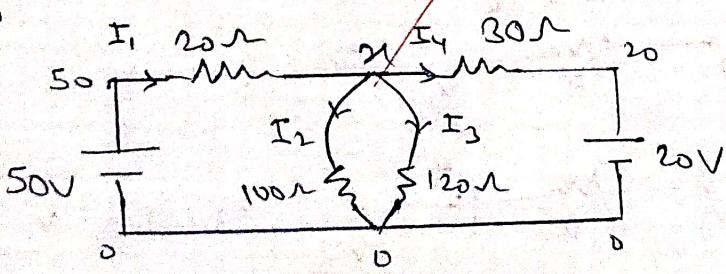

(by KCL)

at node 2

$$I_1 = I_2 + I_3 + I_4$$

$$\frac{x-50}{20} = \frac{x}{100} + \frac{x}{120} + \frac{20-x}{30}$$

$$I_2 = \frac{48-71}{100}$$


$$I_2 = 0.48 \text{ Amp}$$

$$\frac{x-50}{20} = \frac{-6x+5x+400-20x}{60}$$

$$30x - 1500 = +6x + 5x + 400 - 20x$$

$$39x = 1900 \Rightarrow x = 48.71 \text{ V}$$

Q

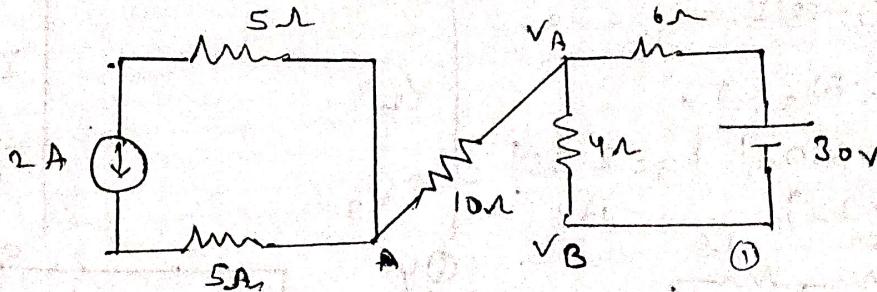

Soln

by derivation of Voltage

loop 1

$$V_{AB} = \frac{4}{4+6} \times 30$$

$$(V_{AB} = \frac{R_{AB}}{R_{\text{eq}}} \times V_{\text{tot}})$$


$$V_{AB} = 12 \text{ Volt}$$

by derivation of Current

$$I_{AB} = \frac{6}{4+6} \times 2 = \frac{6}{5} \text{ Amp.}$$

Practice

Q1

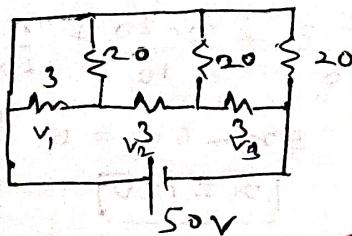

Find voltage across
3Ω resistor.

(KVL)

in loop 1

$$20(I_1 - I_2) + 3(I_1 - I_3) = 0$$

$$23I_1 = 20I_2 - 3I_3$$

$$-3I_4$$

in loop 2

$$20(I_2 - I_3) + 20(I_2 - I_1) + 3I_2 = 0$$

$$43I_2 - 20I_3 - 20I_1 = 0$$


$$-3I_4$$

in loop 3

$$20I_3 + 20(I_3 - I_2) + 3(I_3 - I_4) = 0$$


$$43I_3 - 20I_2 - 3I_4 = 0$$

Q2

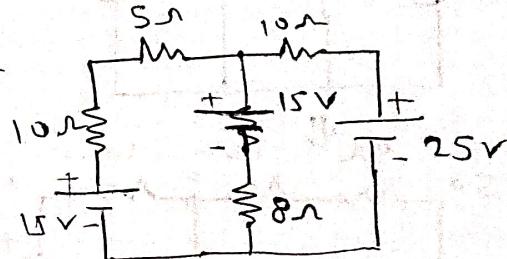

Find the current in

8Ω resistor.

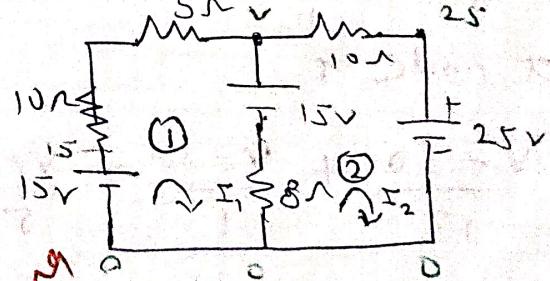

in loop 2

$$5I_1 + 8(I_2 - I_1) + 10I_1 = 15 + 15$$

$$23I_1 - 8I_2 = 0$$

$$I_2 = \frac{23}{8}I_1$$

in loop 2

$$10I_2 + (I_2 - I_1)8 = -25 + 15$$

$$18I_2 - 8I_1 = +10$$

Pakanshe
forming

in loop 2

$$10I_2 + (I_2 - I_1)8 = -25 + 15$$

$$18I_2 - 8I_1 = +10$$

(1)

$$23I_1 - 20I_2 - 3I_4 = 0 \quad (i)$$

$$-20I_2 + 43I_3 - 3I_4 = 0 \quad (ii)$$

$$-20I_1 + 43I_2 - 20I_3 - 3I_4 = 0 \quad (iii)$$

$$9I_4 - 3I_1 - 3I_2 - 3I_3 = 50 \quad (iv)$$

by eq (iii) & (iv)

$$\begin{array}{r} -20I_2 = 3I_4 - 23I_1 \\ -20I_2 = -43I_3 + 3I_4 \\ \hline + \quad \quad \quad + \quad \quad \quad - \\ \cdot 43I_3 = 23I_1 \end{array} \quad (v)$$

$$(I_1 = 1.86I_3)$$

by eq (ii) & (iv)

$$\begin{array}{r} -60I_1 + 129I_2 - 60I_3 - 9I_4 = 0 \\ + 9I_4 - 3I_1 - 3I_2 - 3I_3 = 50 \\ \hline -63I_1 + 126I_2 - 63I_3 = 50 \end{array}$$

by eq (v)

~~$$-63 \times 1.86I_3 + 126I_2 - 63I_3 = 50$$~~

$$-180.18I_3 + 126I_2 = 50 \quad (vi)$$

Now by eq (v) & (vi)

$$\begin{array}{r} -180.18I_3 + 1.59 \times 129I_3 = 50 \\ -180.18I_3 + 205.17I_3 = 50 \end{array}$$

$$24.99I_3 = 50$$

$$I_3 = 2.08A$$

(2) $I_2 = \frac{23}{8}I_1 \quad (i)$, $18I_2 - 8I_1 = 50 \quad (ii)$

by eq (ii)

$$18 \times \frac{23}{8}I_1 - 8I_1 = 50$$

$$(51.75 - 8I_1) = 50$$

$$I_1 = \frac{10}{43.75}$$

$$I_1 = 0.228 \text{ Amp}$$

by eq (i)

$$I_2 = 0.228 \times \frac{23}{8}$$

$$I_2 = 0.655 \text{ Amp}$$

Current in 8Ω

$$I_8 = I_2 - I_1 = 0.427 \text{ Amp.}$$

by eq (ii) & (i)

$$\begin{array}{r} -20I_2 + 43I_3 - 3I_4 = 0 \\ -20I_1 + 43I_2 - 20I_3 - 3I_4 = 0 \\ \hline - + - + \end{array}$$

$$20I_1 + 63I_2 + 63I_3 = 0$$

by eq (v)

$$20 \times 1.86I_3 - 63I_2 + 63I_3 = 0$$

$$(37.2 + 63)I_3 - 63I_2 = 0$$

$$100.2I_3 - 63I_2 = 0$$

$$1.59I_3 = I_2 \quad (vii)$$

by eq (vii)

$$I_2 = 1.59 \times 2.55$$

$$I_2 = 4.05 \text{ Amp}$$

by eq (viii)

$$I_1 = 1.86 \times 2.55$$

$$I_1 = 4.74 \text{ A}$$

by eq (ix)

$$9I_4 = 50 + 3 \times 4.74 + 3 \times 4.05 + 3 \times 2.08$$

$$I_4 = \frac{50 + 14.22 + 12.15 + 6.24}{9}$$

$$I_4 = \frac{82.61}{9} = 9.17 \text{ Amp}$$

$$I_4 = 9.17 \text{ Amp}$$

Now Voltage in 3 Ω resistors

$$V_1 = \frac{(I_4 - I_1)3}{3} =$$



$$V_1 = 13.29 \text{ V}$$

$$V_2 = (I_4 - I_2) \times 3$$

$$V_2 = 15.36 \text{ V}$$

$$V_3 = (I_4 - I_3)3$$

$$V_3 = 21.27 \text{ V}$$

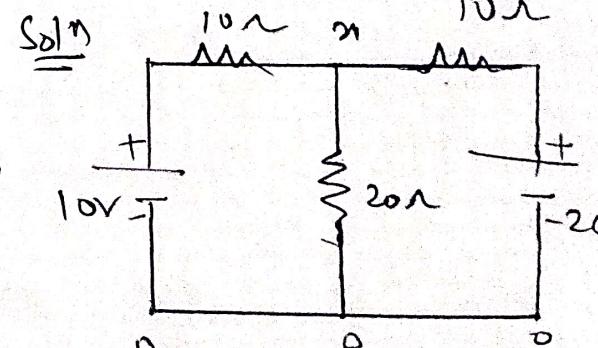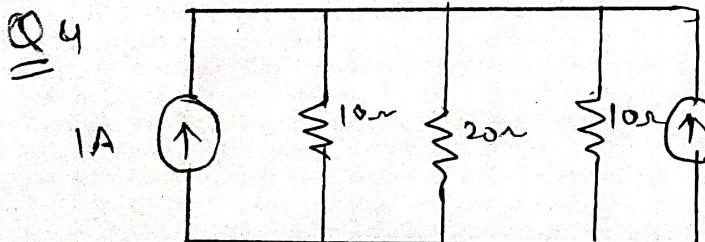

determine the current in 20Ω resistor by nodal analysis at Node α

$$\frac{x-10}{10} + \frac{x-20}{10} + \frac{2}{20} = 0$$

$$I_{20} = \frac{12}{20}$$


$$I_{20} = 0.6 \text{ Amp}$$

$$5x - 60 = 0$$

\leftarrow


$$x = 12 \text{ V}$$

Q2

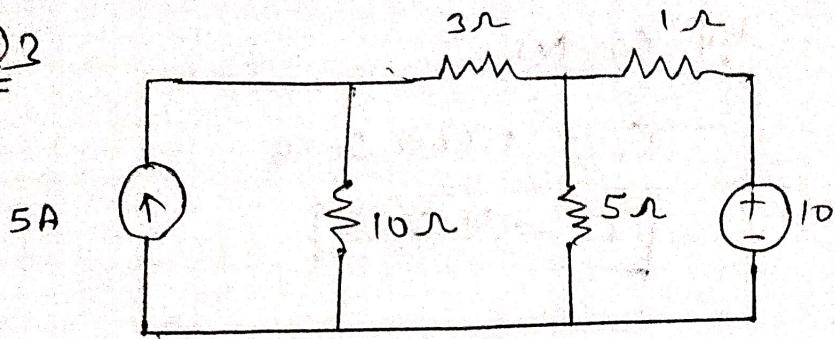

write the node voltage equation & determine the current in branch

Soln

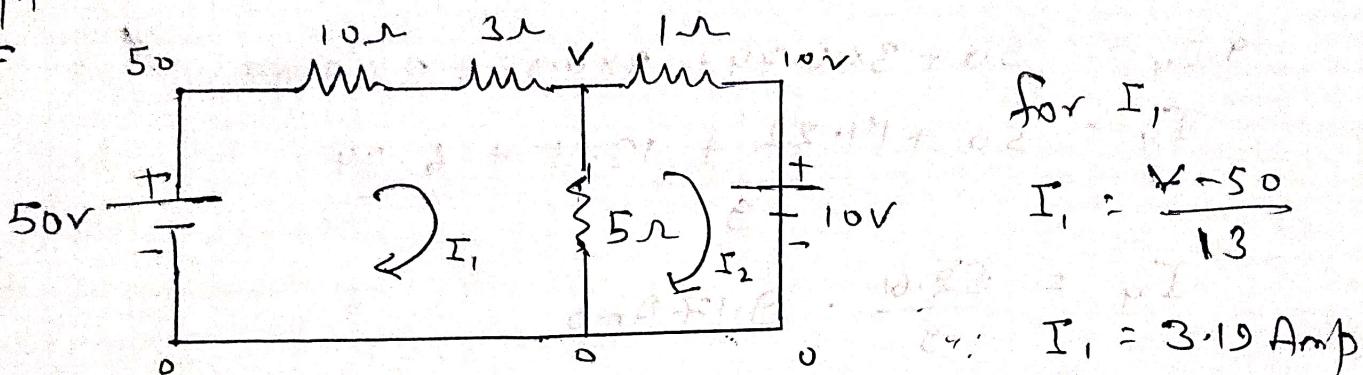

for I_1 ,

$$I_1 = \frac{V - 50}{13}$$

$$\therefore I_1 = 3.19 \text{ Amp}$$

at node V

$$\frac{V - 50}{13} + \frac{V - 10}{1} + \frac{V}{5} = 0$$

$$5V - 250 + 65V - 650 + 13V = 0$$

for I_2

$$I_2 = \frac{8.43 - 10}{1}$$

$$I_2 = 1.57 \text{ Amp}$$

$$83V - 700 = 0$$

$$\boxed{V = 8.43 \text{ Volt}}$$

$$\text{So } I_{10} = I_3 = 3.19 \text{ A}$$

$$I_5 = I_1 - I_2$$



$$= 1.62 \text{ Amp}$$

$$I_{11} = 1.57 \text{ Amp}$$


* Superposition principle *

In a linear electrical network having more than 1 s. independent energy sources, the response in any branch is equals to the algebraic sum of all the responses due to each individual source acting alone.

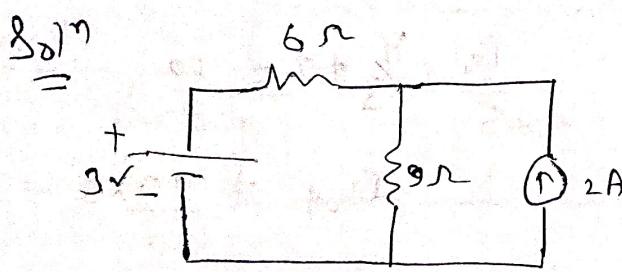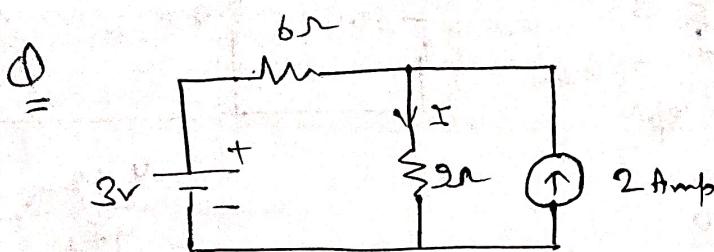→ When voltage source is removed, that branch should be treated as short and for Current Source, branch should be treated as open.




(i) removing the current source

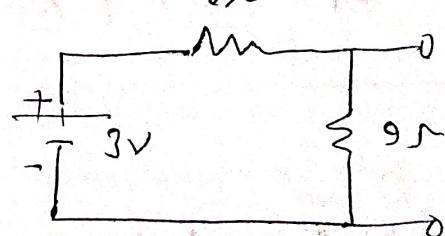

$$I_V = \frac{3}{15} = \frac{1}{5} = 0.2 \text{ Amp}$$

(ii). by removing the voltage source

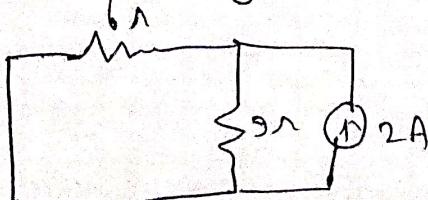


$$I_{eq} = \frac{6 \times 9}{15} = \frac{54}{15} = 3.6 \text{ Amp}$$

$$I_A = \frac{6}{9+6} \times 2 = \frac{6}{15} \times 2 = \frac{4}{5} = 0.8 \text{ Amp}$$


So total current in 9Ω = $0.8 + 0.2 = 1 \text{ Amp}$

Q2

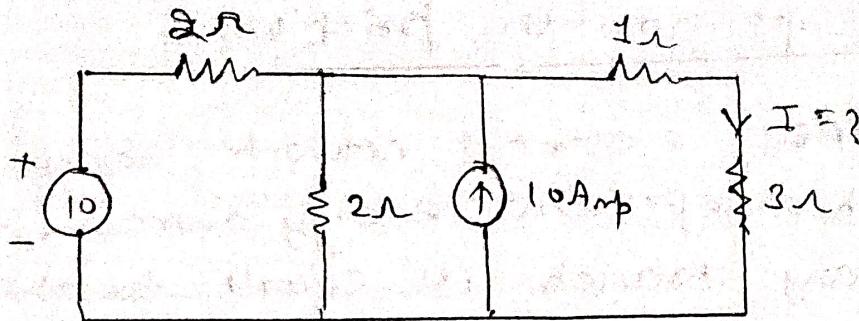

Soln

by removing voltage source

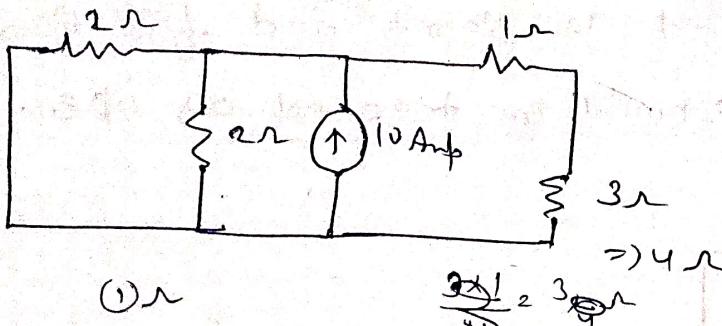

$$I_3 = \frac{10}{2+1} = \frac{10}{3}$$


$$I_{31} = 2 \text{ Amp}$$

Total current in 3Ω

$$= 4 \text{ Amp} = 3 \text{ Amp}$$

by removing voltage source

Current source

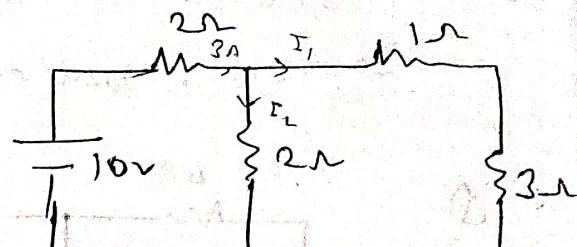

$$\frac{4 \times 2}{4+1} = \frac{4 \times 2}{5}$$

$$R_{eq} = \frac{4}{3} + 2 = \frac{10}{3} \Omega$$


$$I_{tot} = \frac{10 \times 3}{10} = 3 \text{ Amp}$$

$$I_{32} = \frac{2}{5} \times 3$$


$$I_{32} = \underline{\underline{Amp}}$$

Thevenin's theorem

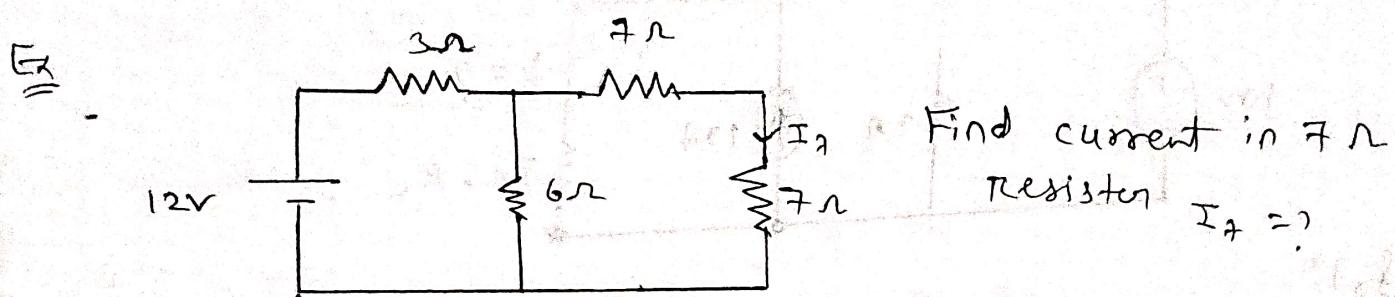* Statement Any two terminals linear active electrical network can be replaced by an ideal voltage source V_{th} in series with a resistance R_{th} . where V_{th} is the open circuit voltage across two terminals. & R_{th} is the equivalent resistance of the network from the two terminals.



Soln = eq circuit

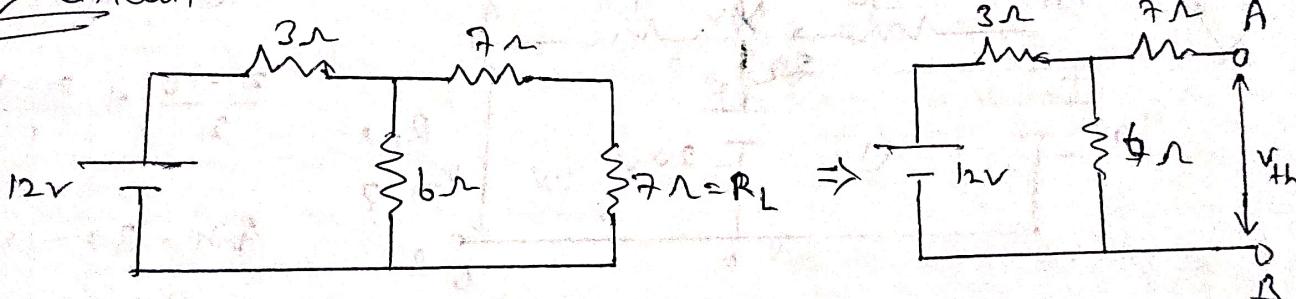


Firstly we have to calculate V_{th} & R_{eq}

$$V_o = V_{th} = 12 \times \frac{6}{6+3} = \frac{12 \times 6}{9} = 8V$$

$$V_o = V_{th} = 8V$$

for R_{eq}

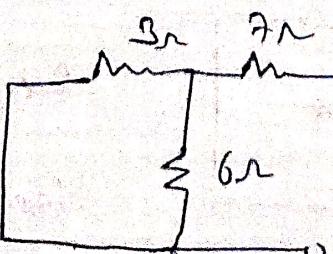
remove all voltage sources & current circuit.




$$\begin{aligned} R_{eq} &= \frac{3 \times 6}{3+6} = 2 + 7 \\ &= 9\Omega \end{aligned}$$

$$R_{eq} = 9\Omega = R_{th}$$


Now eqⁿ circuit \Rightarrow

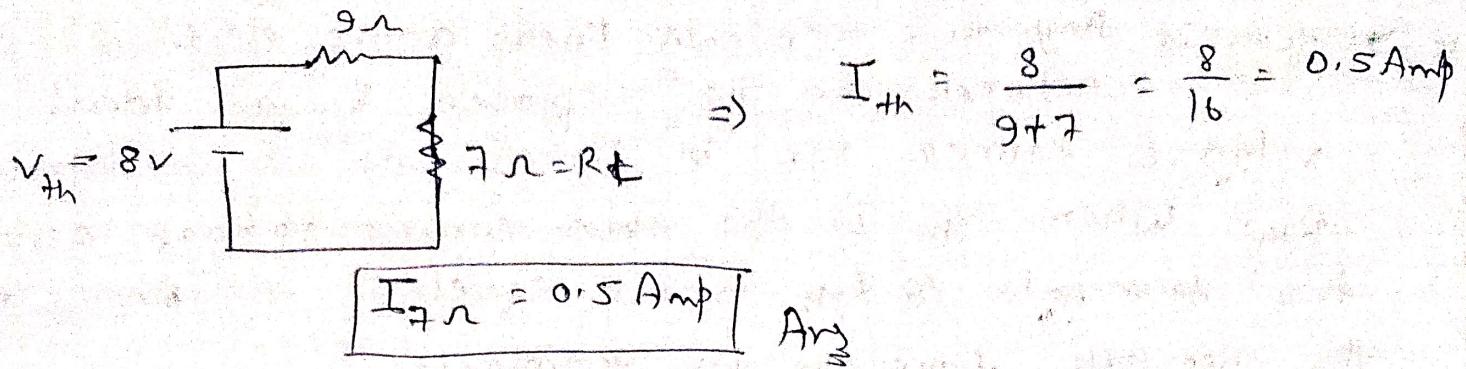

Q

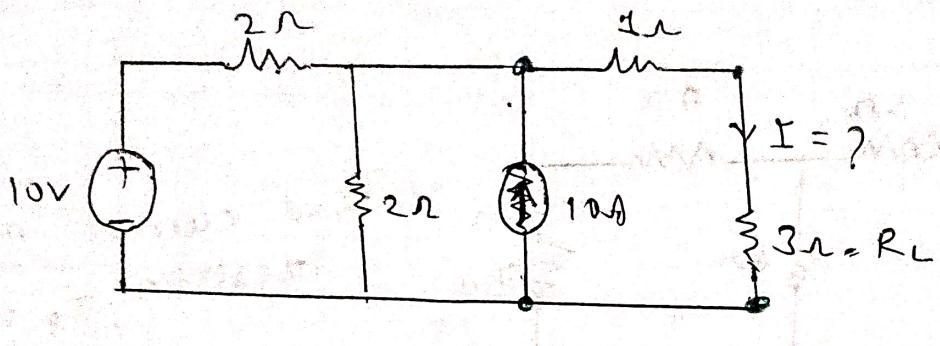

Solⁿ

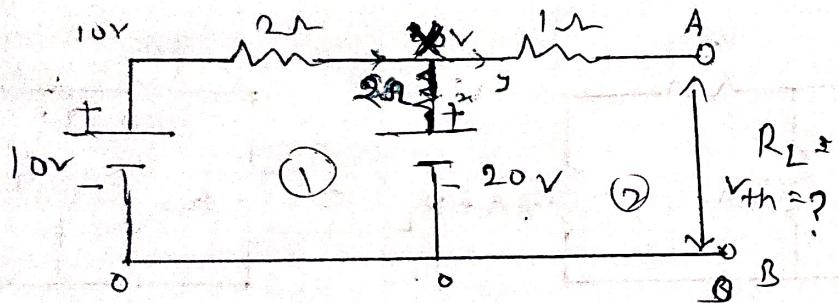

$$\frac{x-10}{2} + \frac{x-V}{1} + \frac{V-20}{2} = 0$$

$$4x - 30 - 2V = 0$$

$$2x - V = 30 \rightarrow J,$$

$$V_{AB} = ?$$

$$I_{tot} = \frac{10}{2} = 5 \text{ Amp}$$


$$\frac{V_A - 20}{1} = 5$$

$$I_1 = \frac{20}{2} = 10 \text{ Amp}$$

$$VA = 15 \text{ Volt} = V_{th}$$

$$I_2 = 5 \text{ Amp}$$

Removing V_{source}


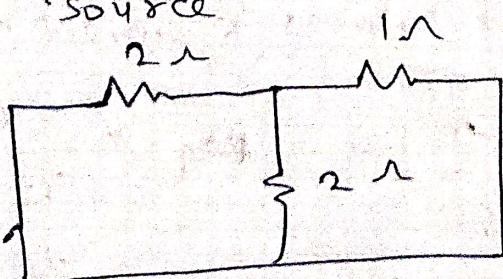


$$R_{eq} = 2\Omega$$

$$\text{Hence } R_{th} = 2+3 = 5\Omega$$

$$I = \frac{15}{5}$$

$$I = 3 \text{ Amp}$$

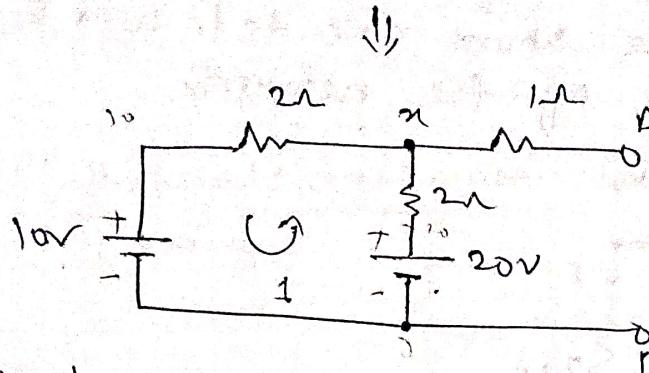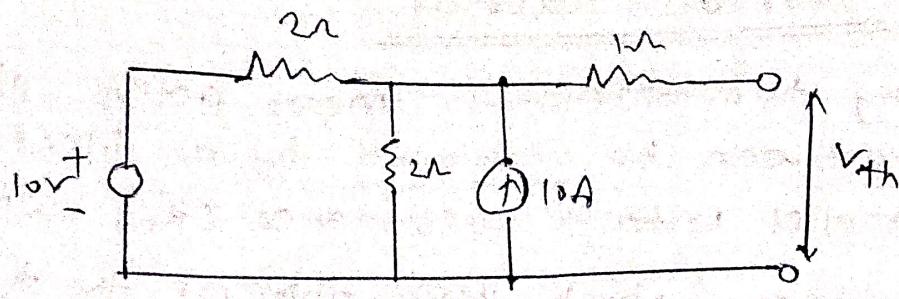

in loop 1

$$2I + I \times 2 = -10 + 20$$

$$4I = 10$$

$$I = 2.5 \text{ Amp}$$

$$R \cdot V_R =$$

$$\frac{20 - 10}{2} = 5$$

$$-x + 20 = 5$$

$$x = 15 \text{ Volts}$$

$$V_{AB} = 15 \text{ Volts}$$

then current


$$I_L = \frac{15}{5} = 3 \text{ Amp}$$

$$R_{eq} = \frac{2+x}{2 \times 2} + 1 = 3 \Omega$$

$$R_{eq} + R_L = 3 + 2 = 5 \Omega$$


Norton's theorem

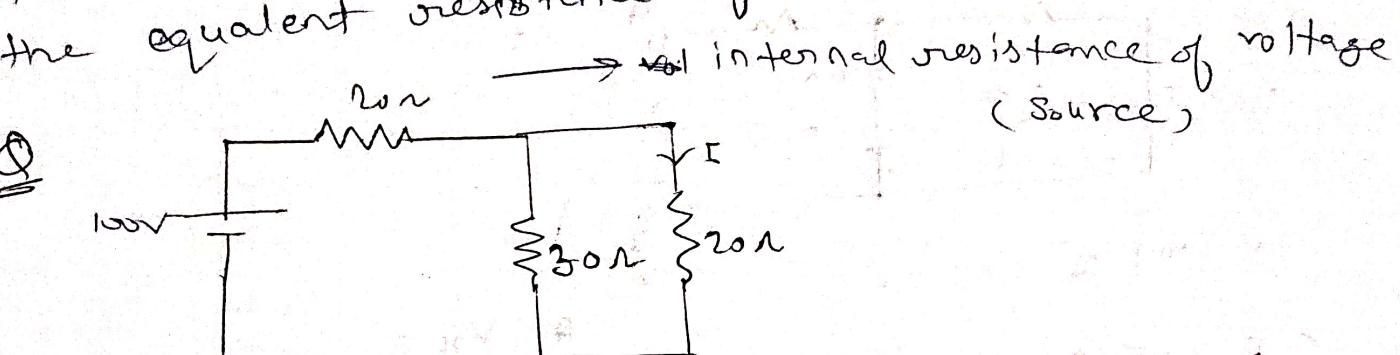* Statement Any two terminals linear active electrical network can be replaced by an ideal current source. In parallel with a resistance (R_n) where I_{in} is the current which flow through the two terminal when they are short circuited, and R_n is the equivalent resistance of the network.




Step 1 $R_L = 20\Omega$


remove R_L from the circuit -

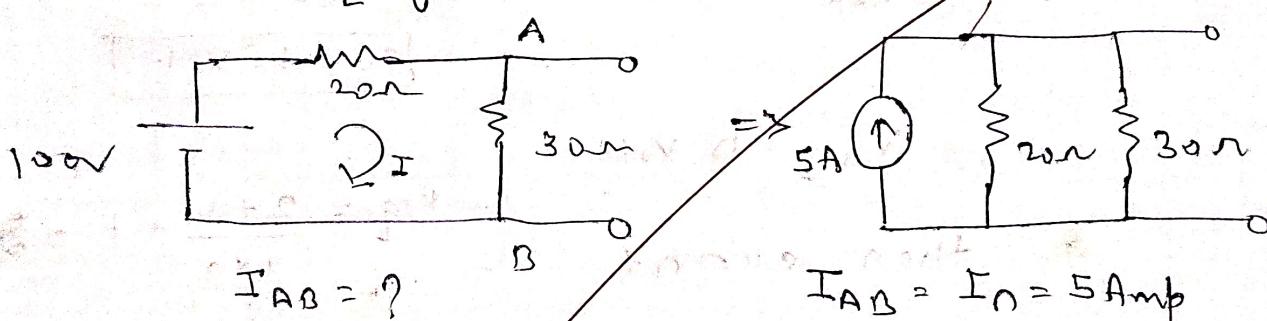

Step 2 remove active element

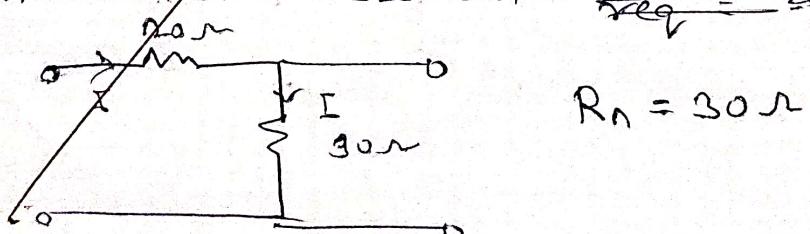

eq circuit -

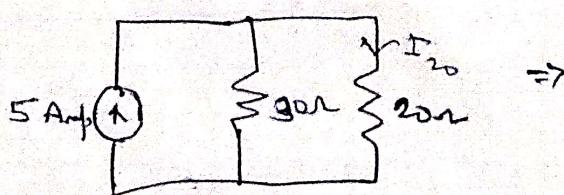


$$I_{20} = \frac{5 \times 30}{50}$$


$$\boxed{I_{20} = 3 \text{ Amp}}$$

Assignment


7

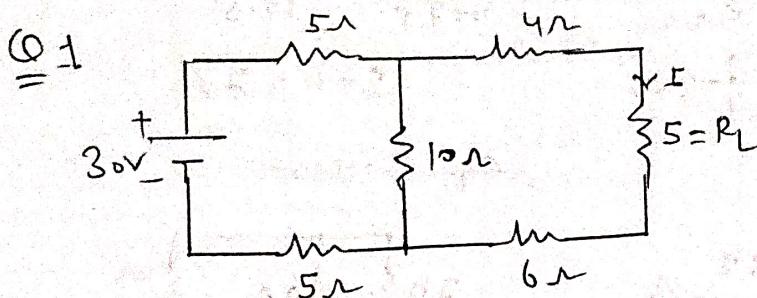

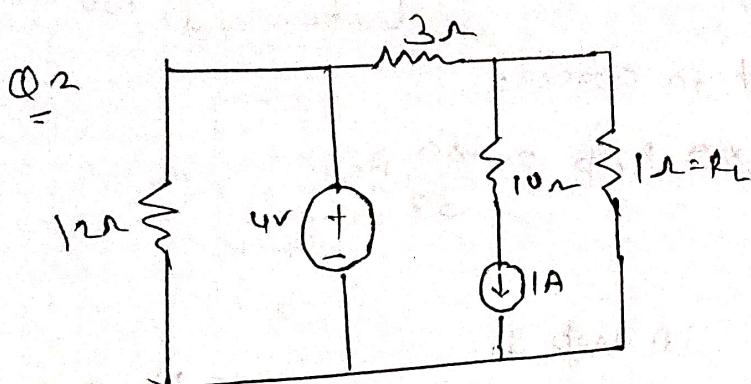Find current through 5Ω resistor by norton's & thvenin's theorem.



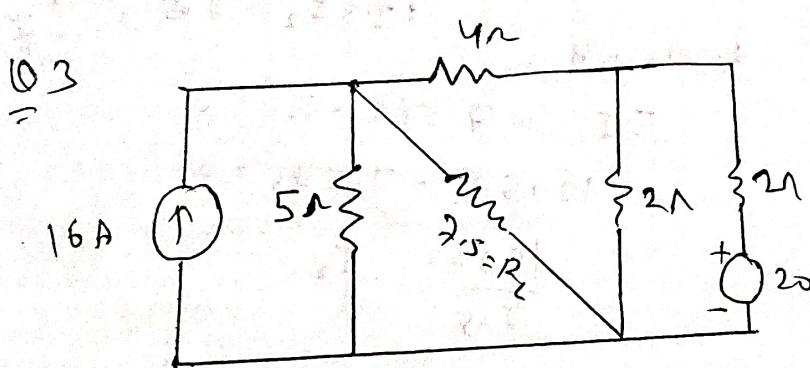
Determine the current through 1Ω resistor through thvenin's & norton's theorem.



Find the current through 2.5Ω resistor by superposition principle.

Solutions

Q3 by removing voltage source

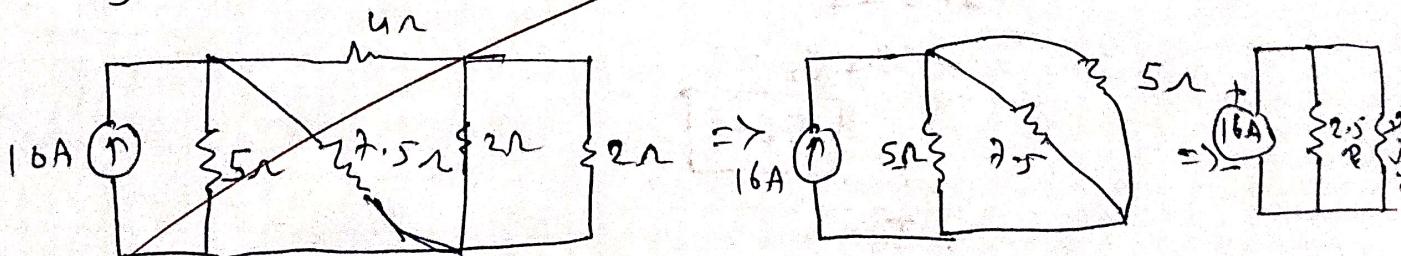


$$R_{eq} = \frac{2.5 \times 7.5}{2.5 + 7.5} = \frac{2.5 \times 7.5}{10} = 1.6 \Omega \quad \text{So } I_{L1} = \frac{2.5}{7.5 + 2.5} \times 16$$

$$I_{L1} = 4 \text{ Amp}$$

30Amp

Step 2
by removing current source

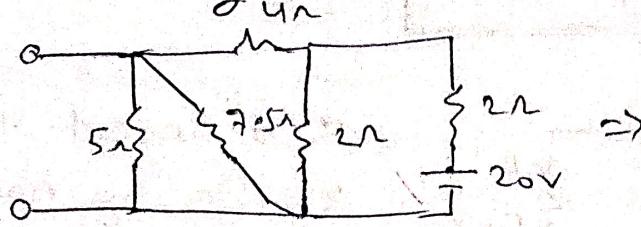


$$\frac{5 \times 7.5}{5+7.5} = \frac{5 \times 7.5}{12.5} = 3\Omega$$

$$3 + 4 = 7\Omega$$

eq Circuit

$$R_{eq} =$$
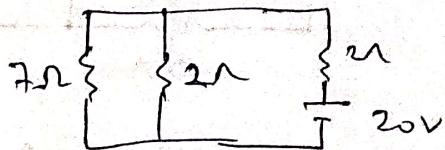
$$R_{eq} = \frac{7 \times 2}{9} + 2 = \frac{32}{9}\Omega$$



So total current in circuit

$$I = \frac{20 \times 9}{32} \text{ Amp} = \frac{180}{32} \text{ Amp}$$

Current division



in loop 1

$$4I_1 + 2I_2 + 7.5(I_2 - I_1) = 0$$

$$13.5I_2 - 7.5I_1 = 0$$

in loop 2

$$5I_1 + 7.5(I_1 - I_2) = 0$$

$$12.5I_1 - 7.5I_2 = 0$$

$$\frac{12.5I_1}{7.5} = I_2$$

$$I_1 = \frac{3}{5}I_2$$

by eq (ii)

$$13.5I_2 - 7.5 \times \frac{3}{5}I_2 = 0$$

$$13.5I_2 - 4.5I_2 = 0$$

$$9I_2 = 0$$


$$I_2 = 0$$

$$I_1 = 0$$

$$\text{So } I_{L2} = 0$$


Hence total current in load R_L is 4 Amp.

Q2 by thevening theorem

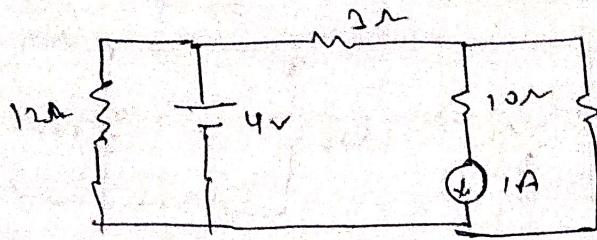


$$R_L = 1\Omega \Rightarrow$$

removing R_L

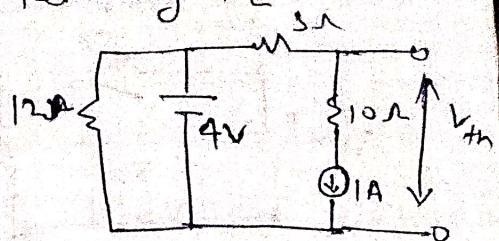


$$V_{th} = 10 \times 1 = 10 \text{ Volts}$$

Now removing all active elements.

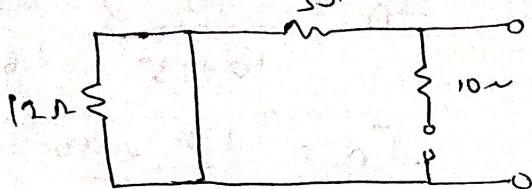

$$R_n = 15\Omega$$

So eq circuit

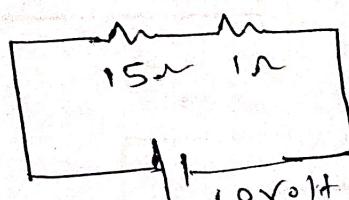


So current in R_L

$$I_L = \frac{10}{15+1} = \frac{10}{16} \text{ Amp}$$

$$I_2 = 0.625 \text{ Amp}$$

by norton's theorem.

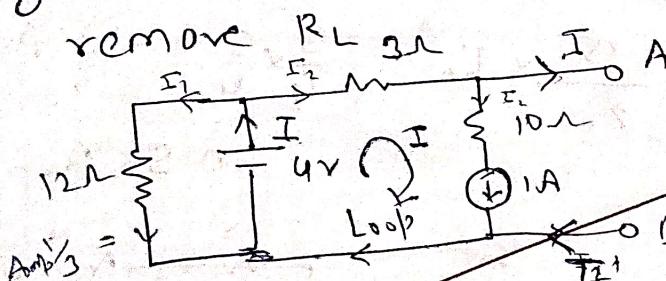

$$\text{in loop } 3I + 10I + 10 = 4$$

$$13I = -6$$


$$I_1 = \frac{4}{12} = \frac{1}{3} \text{ Amp}$$

$$3(I+1) + 10 + 4 = 21$$

$$I+1 = -\frac{6}{13} = -0.46$$


$$I = -2 - 0.46 = -2.46 \text{ Amp}$$
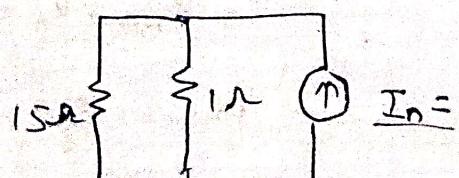
$$R \text{ or } R_{eq} = 15\Omega (12+3)$$




$$I_L = \frac{15}{16} \times I_n = \frac{15}{16} \times =$$

Q1 by norton's theorem

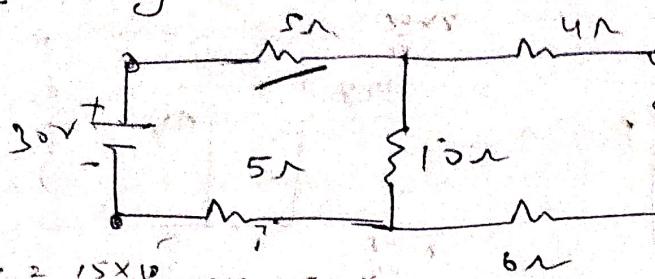

$$R_{eq} = \frac{15 \times 10}{25} = 6\Omega + 5 + 5 = 16\Omega$$

for R_n

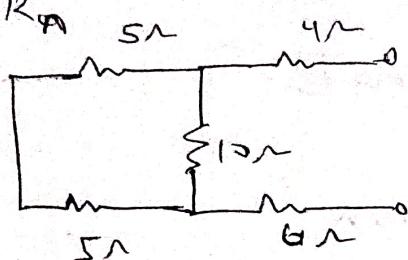

$$R_n = 15\Omega$$

R_{eq} circuit

$$I_{total} = \frac{30}{20}$$


$$I_{total} = \frac{3}{2} \text{ Amp}$$



$$I_L = \frac{15}{20} \times I_n = \frac{3}{4} \times \frac{3}{4} = \frac{9}{16} \text{ Amp}$$

$$0.56 \text{ Amp}$$


by thevenin theorem

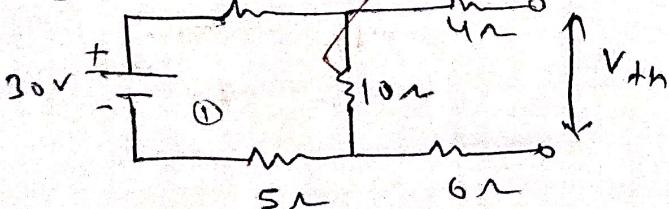

$$I_1 = \frac{30}{20} = \frac{3}{2} \text{ Amp}$$

$$V_{10} = V_{th} = \frac{3}{2} \times 10 = 15 \text{ Volts}$$
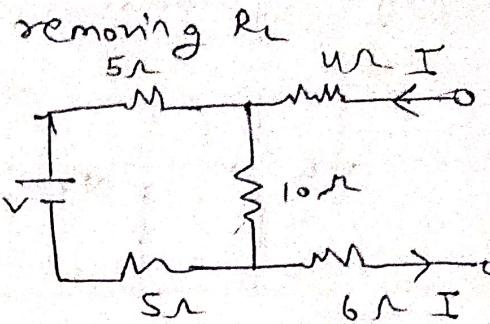
$$I_L = \frac{15}{29} = \frac{3}{4} \quad \leftarrow \\ I_L = 0.75 \text{ Amp}$$



$$\therefore I_{total} = \frac{30}{16} = \frac{3}{2} \text{ Amps}$$


$$I_n = \frac{10}{10+15} \times \frac{30}{16}$$

$$I_n = \frac{10}{25} \times \frac{30}{16} = \frac{3}{4}$$

$$\boxed{I_n = \frac{3}{4} \text{ Amp}}$$


Now eq. circuit

for R_o

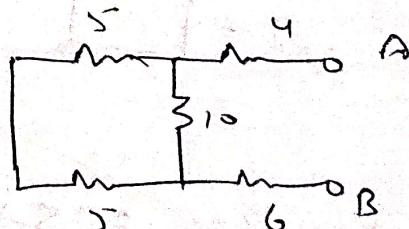


$$R_{AB} = R_n = 15\Omega$$

now eq. circuit

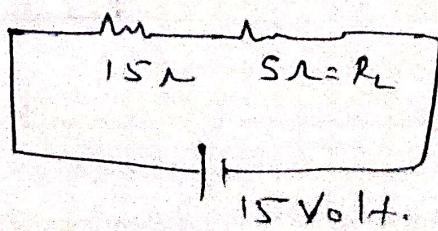

* Max. Power transfer theorem

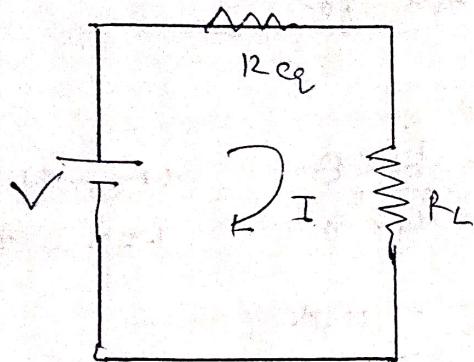⇒ Maximum Power will be transferred from a source network to the load if the load resistance R_L is equivalent to the total resistance of the circuit.



$$I_{\max} = \frac{V}{R_L + R_s}$$

$\therefore R_L = R_s$ (Condition for Max Power)


$$I_{\max} = \frac{V}{2R_L}$$

maximum power will be

$$P_{\max} = I_{\max}^2 R_L$$

$$P_{\max} = \frac{V^2}{4R_L}$$

Ex.

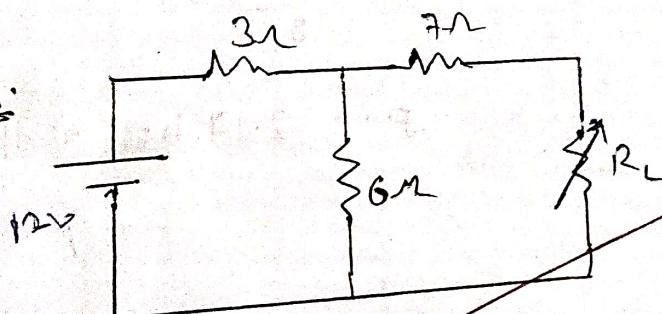



In given circuit what is the max^m Power that can be absorbed by the load resistance R_L . If it varies,


what is the power absorbed by

load R_L if.

$$(i) R_L = 7\Omega \quad (ii) R_L = 11\Omega$$

circuit

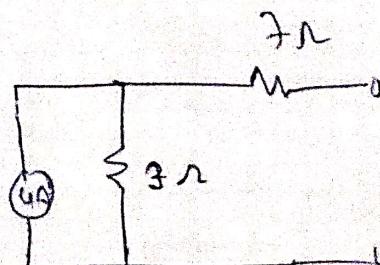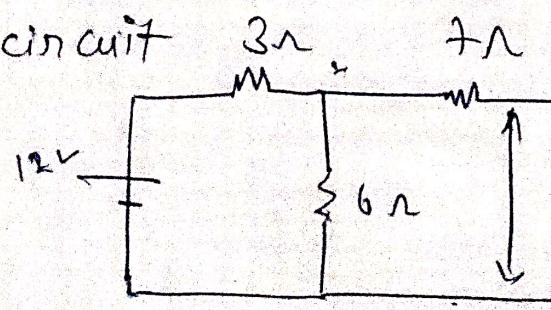

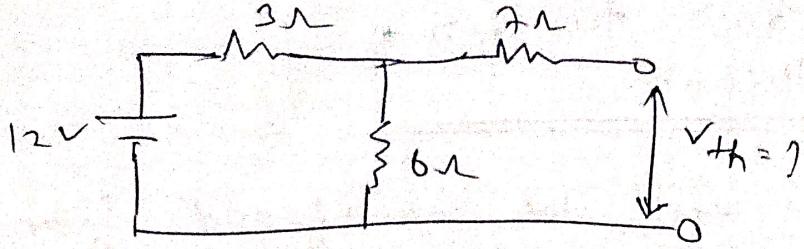

$$V_{th} = \frac{2}{9} \times 12$$

$$V_{th} = 8 \text{ volt}$$

$$R_{eq} = 3 + 6 = 9 \Omega$$

Condition for max power transfer

$$R_{eq} = R_L = 9 \Omega$$

$$P_{max} = \frac{V^2}{4R_L} = \frac{8^2}{4 \times 9} = 4 \text{ watt}$$

$$(i) R_L = 7 \Omega$$

$$I = \frac{V}{R} = \frac{V}{R_L + R_S}$$

$$= \frac{8}{9+7}$$

$$I_{max} = \frac{1}{2} \text{ Amp}$$

$$(ii) R_L = 11 \Omega$$

$$I = \frac{8}{11+9} = \frac{8}{18} = \frac{4}{9}$$


$$P = I^2 R_L$$

$$P = \frac{16}{81} \times 11$$

$$P = I_{max}^2 R_L$$

$$P = 2.17 \text{ watt}$$


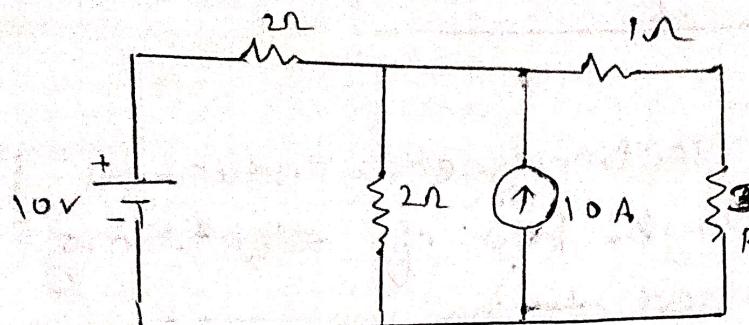
$$P = \frac{1}{4} \times 7 = 1.75 \text{ watt}$$



what the maxⁿ power transferred or absorbed by load resistor if it varies what is the power absorbed by load resistor?

$$R_L = ?$$

by removing R_L

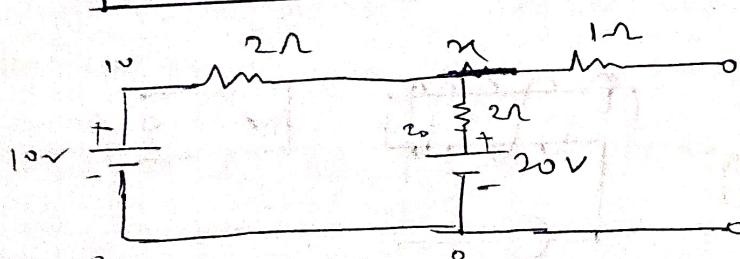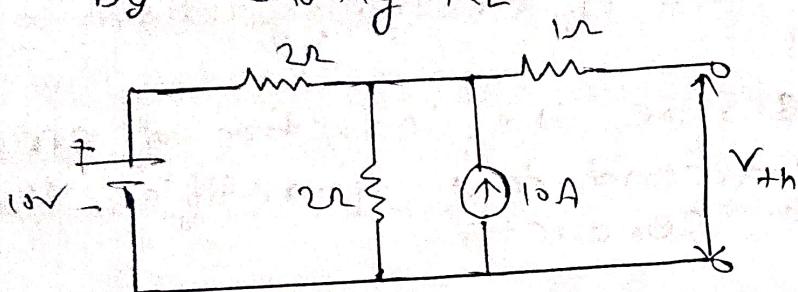


$$\frac{20 - n}{2} + \frac{20 - n}{2} + n = 0$$

$$2n = 30 \text{ Volts}$$

$$n = 15 \text{ Volts}$$

$$V_{Th} = 15 \text{ Volts}$$

for R_{eq} :

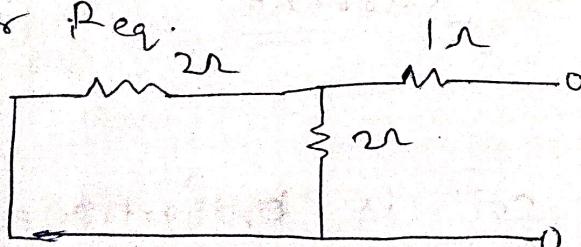

$$R_{eq} = 2\Omega \Rightarrow$$

$$I_{max} = \frac{V}{R_{eq} + R_L} = \frac{15}{2+3} = 3 \text{ Amps}$$

$$P_{max} = I_{max}^2 \times R_L = (3)^2 \times 3 = 27 \text{ watt.}$$

Now

$$P_{max} = \frac{V^2}{4R_L} = \frac{15 \times 15}{4 \times 8} = \frac{225}{8} = 28.125 \text{ watt.}$$


Faraday's Law

→ Faraday's law of electromagnetic induction is also known as Faraday's law of electromagnetism, which help us to predict how a magnetic field interact with an electrical circuit to produce emf. This phenomena is known as electromagnetic induction. Faraday's law of electromagnetism consists of two laws.

The first law describe the induction of emf in a conductor and second law quantifies the emf produced in the conductor.

First law :-

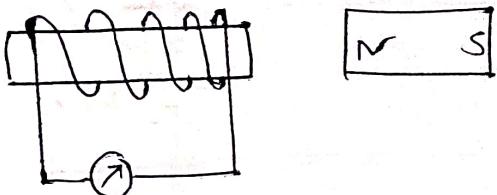Whenever a conductor is placed in a varying magnetic field and an emf is induced.



If the circuit is closed a current is also induced, which is called "induced current".

Second law :-

The induced emf in a coil is proportional to the rate of change of magnetic

$$e = -N \frac{d\phi}{dt}$$

Here

e = induced emf

N = number of turns in a coil or conductor


ϕ = Magnetic flux.

* Lenz's law: The induced

The induced emf with different polarities induce a current whose magnetic field opposes the change in magnetic flux through the loop in order to insure that the original flux is maintained through the loop when current flows through it.

⇒ Lenz's law is the most convenient method to determine the direction of current. It states that the direction of an current is always oppose the change in magnetic flux in the circuit or the magnetic field that produce the induced current.

* Questions on Star - Delta formation.

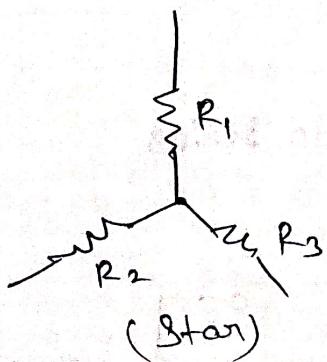


Star → Delta

$$R_{12} = R_1 + R_2 + \frac{R_1 \cdot R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 \cdot R_3}{R_1}$$
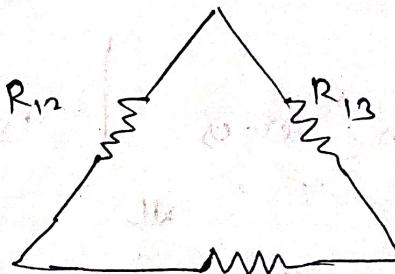
$$R_{31} = R_3 + R_1 + \frac{R_3 \cdot R_1}{R_2}$$




Delta → Star


$$R_1 = \frac{R_{23} \cdot R_{12}}{R_{13} + R_{12} + R_{23}}$$

$$R_2 = \frac{R_{23} \cdot R_{21}}{R_{13} + R_{12} + R_{23}}$$
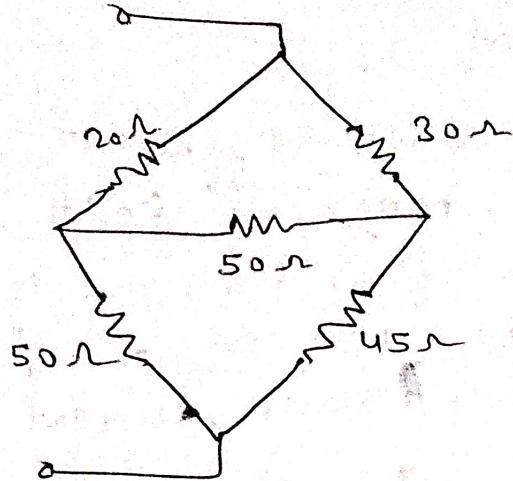
$$R_3 = \frac{R_{32} \cdot R_{31}}{R_{31} + R_{32} + R_{12}}$$




let $\Delta = \square$

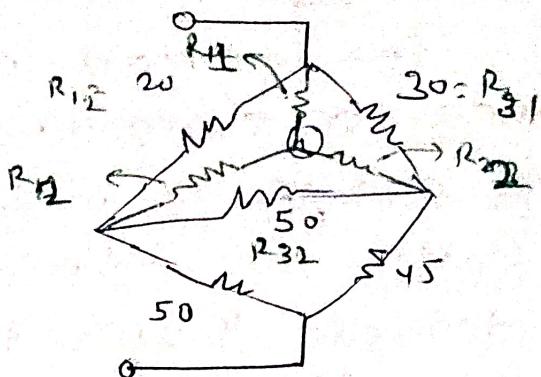

$$R_{12} = \frac{R_{12} \cdot R_{31}}{\epsilon R} = \frac{20 \times 50}{100} = 10 \Omega$$

$$R_2 = \frac{R_{21} \cdot R_{32}}{\epsilon R} = \frac{20 \times 30}{100} = 6 \Omega$$

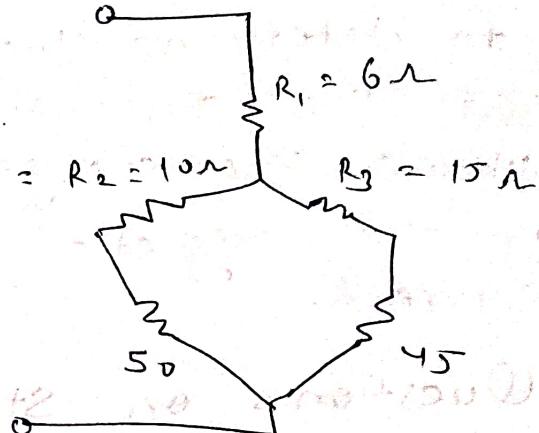
$$R_3 = \frac{R_{31} \cdot R_{21}}{\epsilon R} = \frac{50 \times 20}{100} = 10 \Omega$$



Now

10 & 50 in series


15 & 45 in series

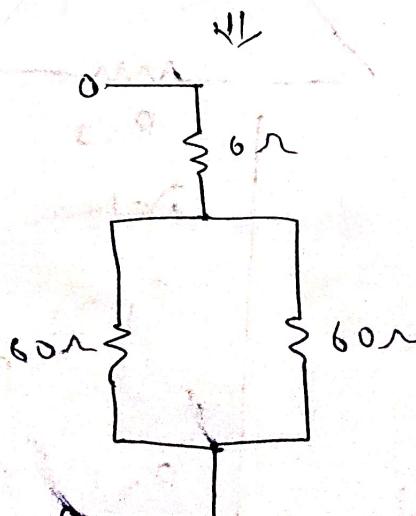




$$\boxed{R_{eq} = 36 \Omega}$$

Ay

Q

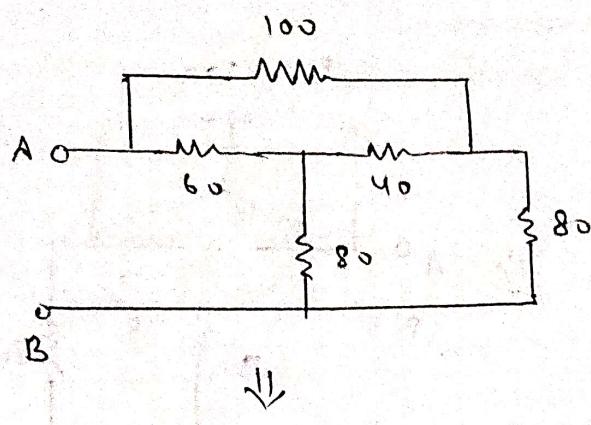

Soln

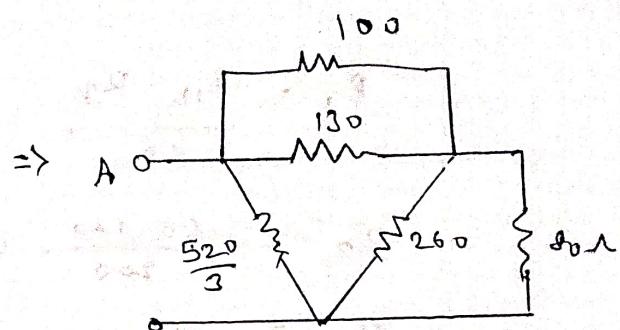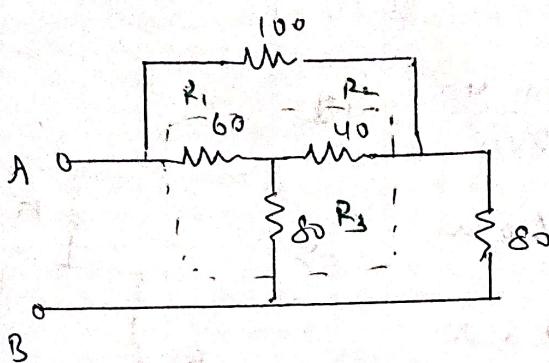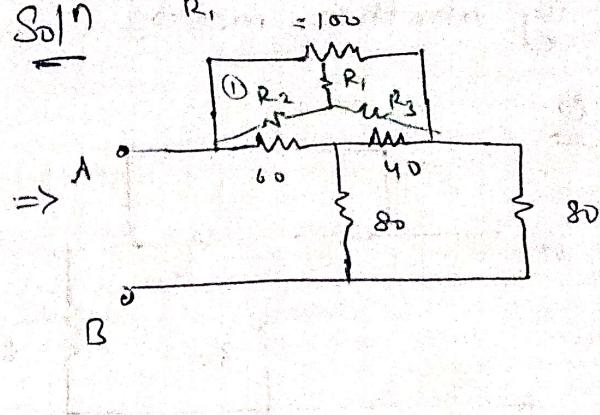

for Star to delta

$$R_{12} = 60 + 40 + \frac{60 \times 40}{80}$$

$$R_{12} = 130 \Omega$$

$$R_{23} = 40 + 80 + \frac{80 \times 40}{60}$$

$$= \frac{520}{3} \Omega$$

$$R_{31} = 60 + 80 + \frac{60 \times 80}{40}$$

$$= 260 \Omega$$

in circuit

100 & 130 in Parallel

$$\text{Req(1)} = \frac{130}{23} \Omega = 5.652 \Omega$$

80 & 260 in Parallel


$$\text{Req(2)} = \frac{1040}{17} \Omega = 61.17 \Omega$$

Now

Req(1) & Req(2) in series

$$\text{Req(3)} = 117.7 \Omega$$

Hence eq. circuit is


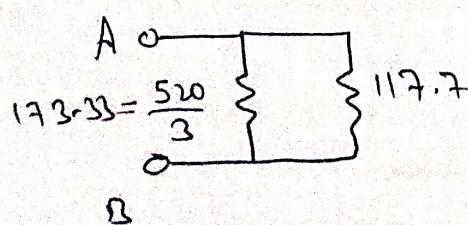


Now Req

$$\text{Req} = \frac{117.7 \times 173.33}{291}$$

$$\text{Req} = 70.09 \Omega \quad \text{Ans}$$



By another method

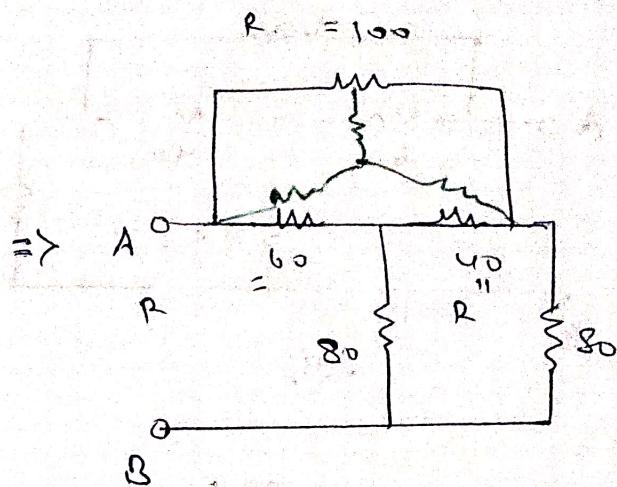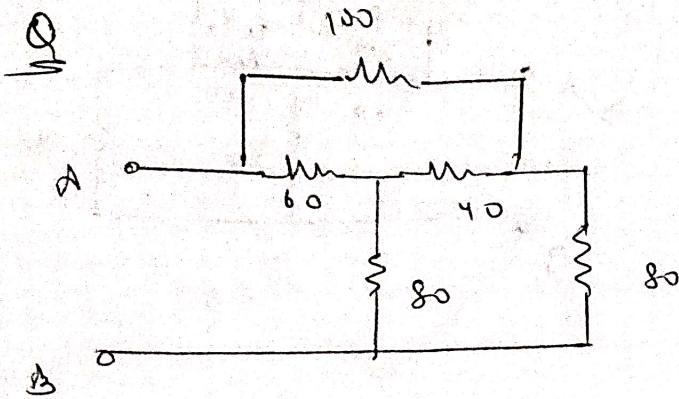

$$R_1 = \frac{R_{12} \cdot R_{31}}{\Sigma R} = \frac{60 \cdot 40}{200} = 12 \Omega$$

$$R_2 = \frac{60 \cdot 100}{200} = 30 \Omega$$
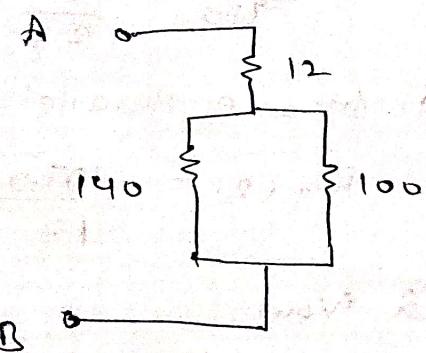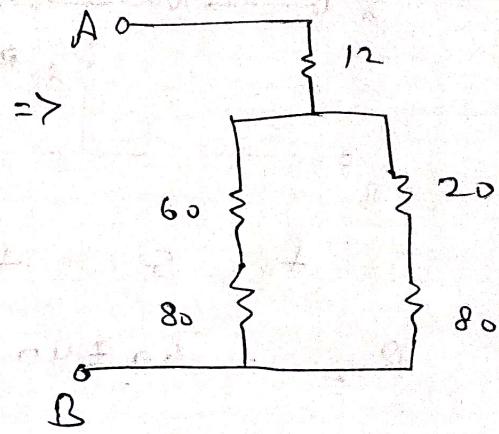
$$R_3 = \frac{40 \cdot 100}{200} = 20 \Omega$$



$$R_{eq} = 12 + \frac{140 \cdot 80}{240}$$


$$R_{eq} = 12 + 58.33$$

$$R_{eq} = 70.33 \Omega$$

Answer


Assignment 2

Q1

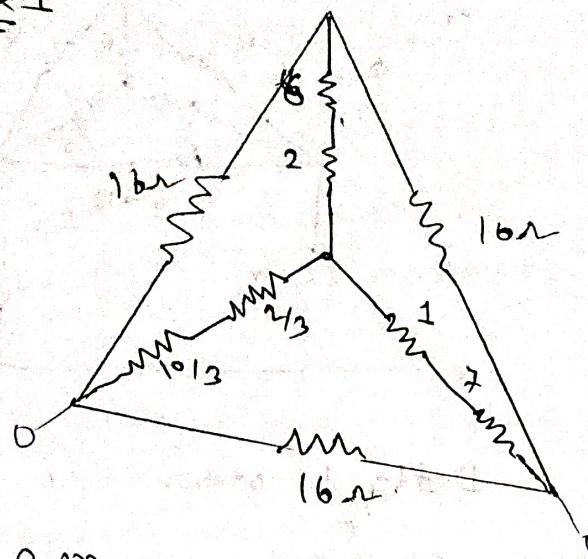


Find the eqa resistance of the circuit using star-delta formation.

Soln

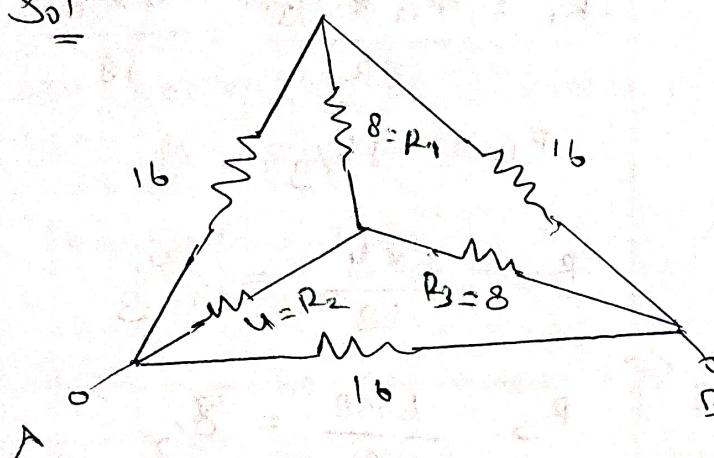

Star to delta

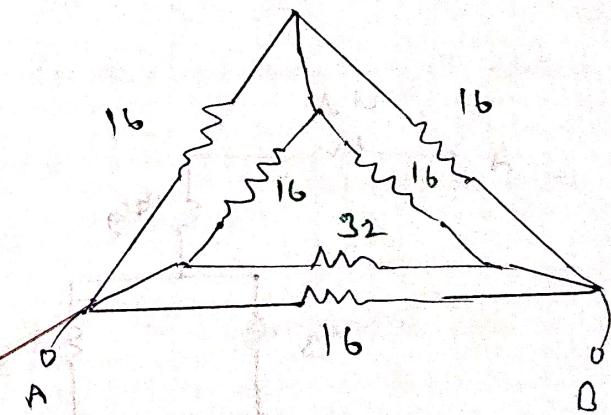


$$R_{12} = \frac{R_1 + R_2 + R_1 \cdot R_2}{R_3}$$

$$R_{12} = 8 + 4 + \frac{8 \cdot 4}{8} = 16 \Omega$$

$$R_{23} = 8 + 4 + \frac{8 \cdot 4}{8} = 16 \Omega$$


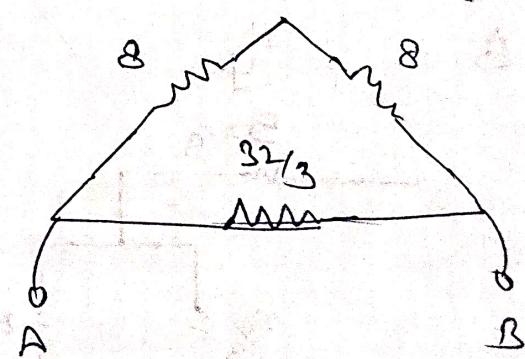
$$R_{31} = 8 + 8 + \frac{8 \cdot 8^2}{4} = 32 \Omega$$



Now 16 & $32/3$ in parallel

$$R_{eq} = \frac{16 \times 32/3}{16 + 32/3} = \frac{32}{5} \Omega = 6.4 \Omega$$

Q2

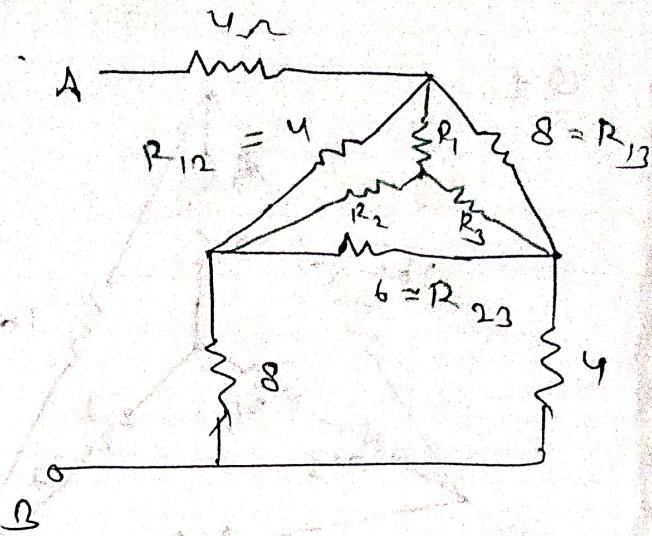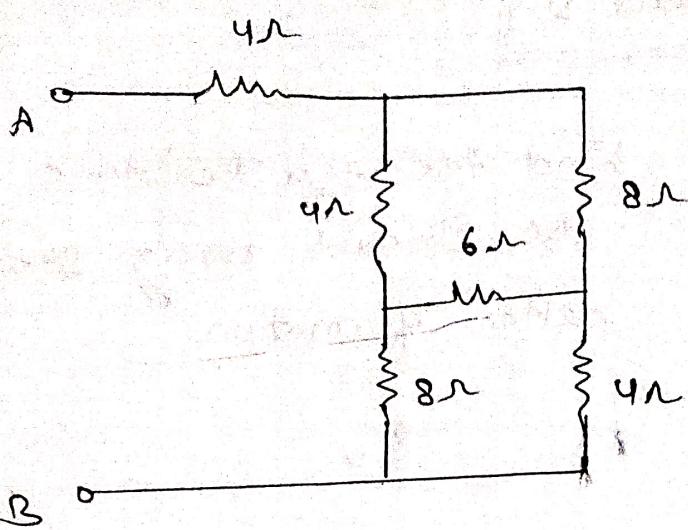



Determine the Req. btw
A & B through star
delta formation.

$$R_1 = \frac{R_{12} * R_{31}}{\Sigma R} = \frac{4 * 8}{18}$$

$$R_1 = 16/9$$

$$R_2 = \frac{6 * 4}{18} = 4/3$$

$$R_3 = \frac{6 * 8}{18} = 8/3$$

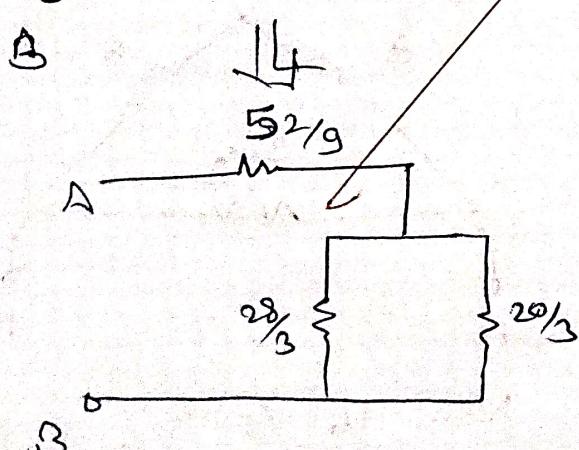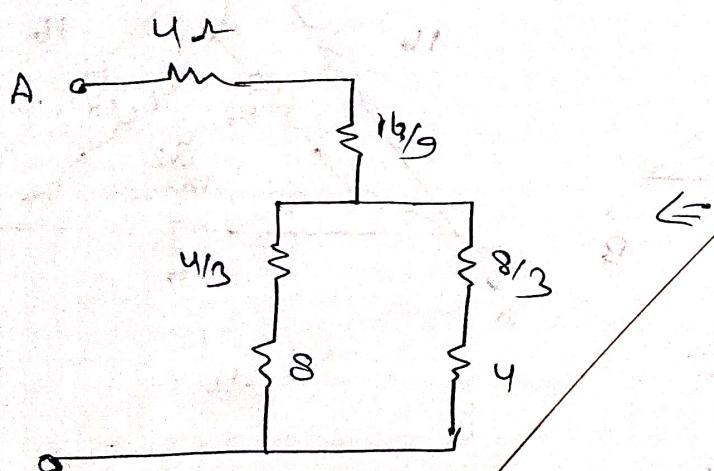

$$\text{Req} = \frac{52}{9} + \frac{\frac{28}{3} \times \frac{20}{3}}{\frac{48}{3} + \frac{16}{3}}$$

$$\text{Req} = (52 + 35) \frac{1}{9}$$

$$\text{Req} = 87/9 = 9.67 \Omega$$

* BEE *

Basic Electronics and Engineering

Basic Terminology of BEE

Electrical energy is energy related to forces on electrically charged particles and the movement of those particles. This energy is supplied by the combination of current and voltage (electric potential difference).

Voltage :-

Voltage is also known as potential difference, electric pressure or electric tension. Voltage is the difference in electric potential between two points of a surface (conductor).

• Electric current:-

Electric current refers to the flow of electrons in an electrical circuit. It is measured in Ampere.

There are two type of current

(i) Static

is Dynamic

DC ← → AC

• Direct current:

(i) Direct current occurs when the current flows in one constant direction. D.C. normally comes from batteries, solar panels, or A.C to D.C converters. D.C. is preferred type of power for all electronic & electrical devices. There is no frequencies in D.C Power.

(ii) Alternating current :-

A.C. current occurs when the electric current changes its direction. A.C. is preferred type of power that is delivered to homes and business through transmission lines.

RESISTOR :-

A resistor represents a given amount of resistance in a circuit. Resistance is a property of resistor that oppose the flow of current. Resistance is measured by 'Ohms' (Ω) by the ohm's law

$$\therefore V = IR$$

$$R = \frac{V}{I}$$

Symbol -

Ohm is represented by Omega symbol. (Ω)


CAPACITORS :-

A capacitor is a device that is used to store charge in electric form. This property is known as capacitance of capacitor. The charge that is stored in capacitor is measured by Coulomb and the unit of capacitor is Farad.

$$\text{Symbol} - \parallel \text{ or } \cap \quad C = \frac{Q}{V}$$

INDUCTORS :-

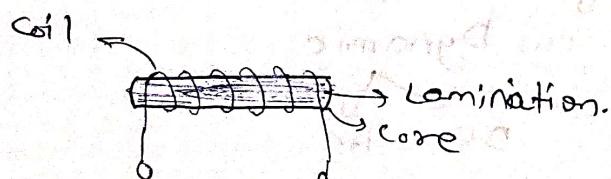Inductor is a coil that is used to store charge in magnetic form. Inductors are used in electronic circuit to oppose the change in electric current.




Unit \rightarrow Henry.

$$L = \frac{\phi}{I}$$

where ϕ = flux

L = inductance.

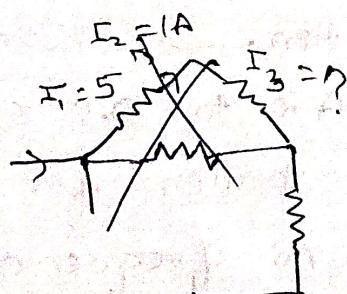

node 1


$$I_1 + I_2 + I_3 = I_5 + I_4$$

$$5 + 1 + 1 = I_5 + I_4$$

$$I_5 = 8A$$

$$I_5 = 4A_{\text{mp}}$$

~~$I_2 = I_3 = 1A$~~

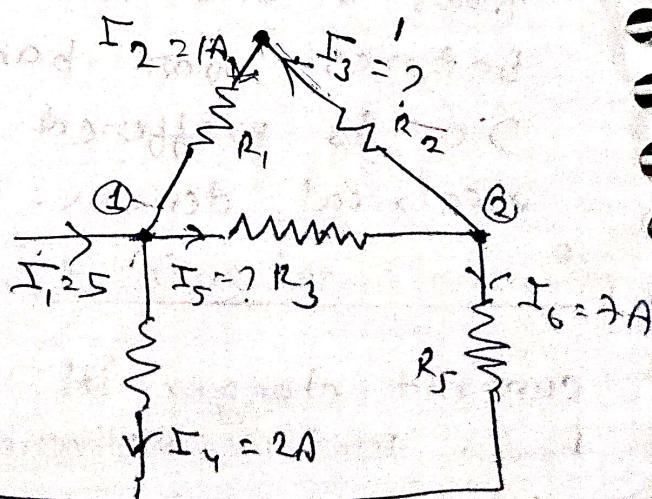

Fundamentals

Current flow: -

Current flow basically means the flow of electric charges with respect to time.

In a electric circuit, when the electric charge is flowing in one direction, the current will flow in the opposite direction. The electric current flow starts from the negative terminal to the positive terminal of the battery, as the electron will flow from the positive terminal to the negative terminal.

From ohm's law, the expression for current is

$$V = IR$$

Here V is the voltage of the battery, R is the resistance connected in the circuit, and I is the current flow in the circuit.

From ohm's law the current can be defined as the voltage through the circuit per unit resistance.

The unit of current is Ampere (A).

When the current flow through the circuit, it causes heating in that device; as a result, we can get light in an incandescent light bulb. The heating is known as "Joule heating".

Current is of two types:

- DC Current
- AC Current

DC Current:

DC current which is created from a DC voltage

Source.

• AC Current :-

AC Current which is created from AC Voltage Source.

In an atom the number of neutrons and protons are same. Basically, an atom is electrically neutral. The electrons near the nucleus are strongly bounded and the outer electrons are loosely bounded. The loosely bounded electrons may be detached from the atoms. Now, when the external voltage applies, the loosely bounded electrons come out from the orbit and start drifting toward a direction according to the direction of the applied voltage and electric field. This causes a flow of current through the circuit.

x [Current flow basically means the flow of electric charges with respect to time. In an electric circuit when the electric charge is flowing in one direction, the current will flow in the opposite direction.] x

Q what causes current to flow?

Ans An electrical phenomenon is caused by flow of free electrons from one atom to another. The characteristics of current electricity are opposite to those of static electricity, wires are made up of conductors such as copper or aluminium.. Current flow from (+) to (-)ve and e⁻ flows from (-)ve to (+)ve. Why current flow from (-)ve to (+)ve...? because the e⁻ always move towards the (+)ve attractor, current (+)ve attractor, the holes will tends to flow to the negative. Hole flow is usually called "conventional current". Flow from (+)ve to (-)ve, e⁻ flow goes in the reverse direction, from (-)ve to (+)ve

Q What is current; explain?

Current is a flow of electrical charge carriers, usually electrons or electronegative atoms.

Electric current can be either direct or alternating.

Direct current (DC) flows in the same direction at all points in time, although the instantaneous magnitude of the current might vary.

Q What is current & voltage?

Current is the rate at which electric charge flows past a point in a circuit. In other words, Current is the rate of flow of charge.

Voltage, also called electromotive force is the potential difference in charge between two points in an electrical field.

Q What is current and its types?

There are two types of current : direct & Alternating
In a direct current, abbreviated DC, the electrons move in one direction.

In a Alternation, abbreviated AC, the direction of current should fluctuate.