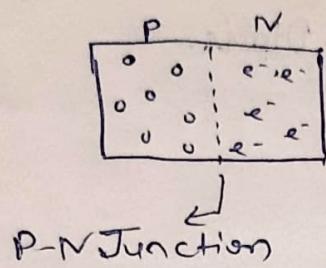


Unit - 5


Power Converter

Forward bias P-N Junction Diode:-



P-N Junction

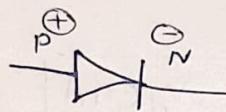
hole e^- \Rightarrow Diffusion current \Rightarrow momentary motion of electron.



Diode \Rightarrow Combination of P-N semi-

P type & N type semiconductor.
(Low voltage device)

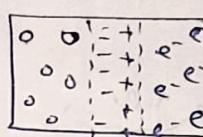P-N-Junction \Rightarrow Separation of boundary of P and N semiconductor.



Depletion layer (d)



Potential barrier

$$V = \frac{E}{d} C$$

In forward bias


\rightarrow diode is active. -

\rightarrow current flows. -

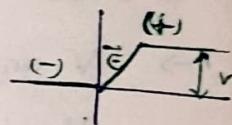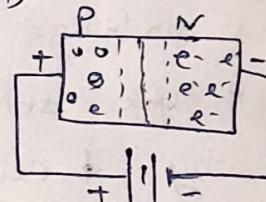

in forward bias, depletion layer will decrease when it's connected to the external supply.

N type is heavily doped.

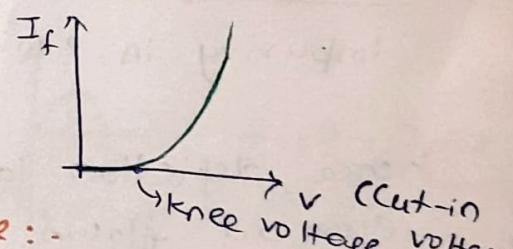



Reverse bias P-N Junction Diode:-

Diode is not active

No current flow.


\rightarrow Depletion layer will increase

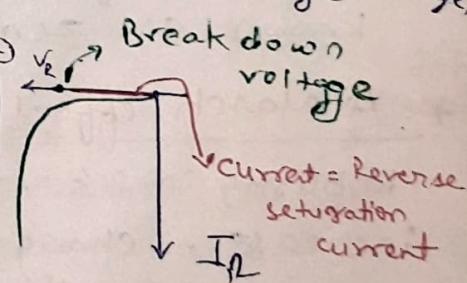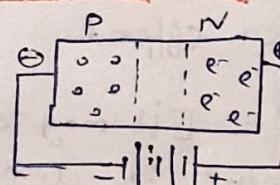\rightarrow Break down voltage \Rightarrow Current sudden increase at that voltage.




Peak inverse voltage :- max value of reverse voltage that a diode can bear, is called peak inverse voltage. Upto this voltage a diode can not be damaged.

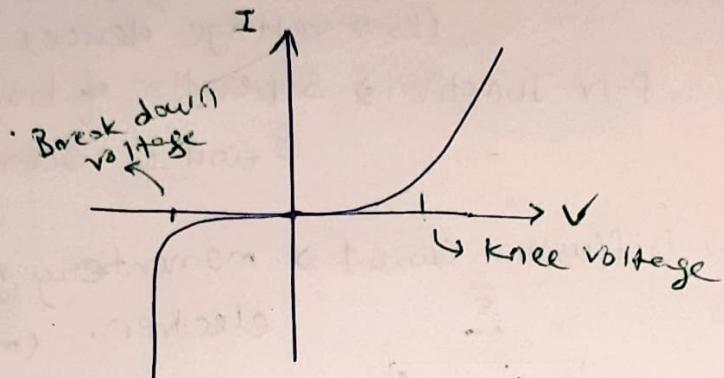V-I Characteristics of PN Junction Diode.



Zener Diode

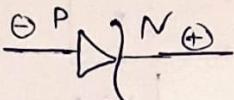

$$I_J = v_d \text{ enA}$$

- always connected in reverse biased.
- Used as voltage Regulator.
- N and P type semiconductor are heavily doped that why current flows through the minority charge carriers.

* Zener effect

impurity in P & N ↑ ⇒ minority charge carriers will increase

hence depletion layer will decrease ~~so~~ that's why the current flows in Reverse biased. This effect is known as zener effect. [at low potential]


* Avalanche effect:- [it may destroy device]

impurity in P & N type is decreasing, depletion layer will increase, charge carriers have maximum energy then it will break bonds and produce free charge carriers. It is called Avalanche effect [at high Potential]

Application of Zener diode

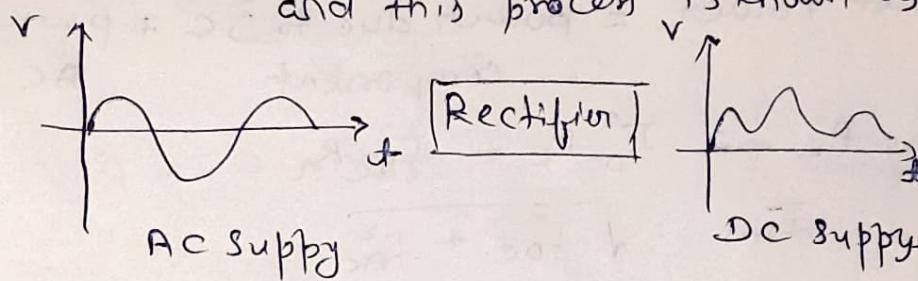1. As a voltage regulator
2. As a reference voltage device.
3. Constant current source with transistor
4. Over voltage protection

Rectifier:- It converts AC current into DC current and this process is known as Rectification.





Rectifier

Half wave Rectifier
(HWR)


full wave Rectifier
(FWR)

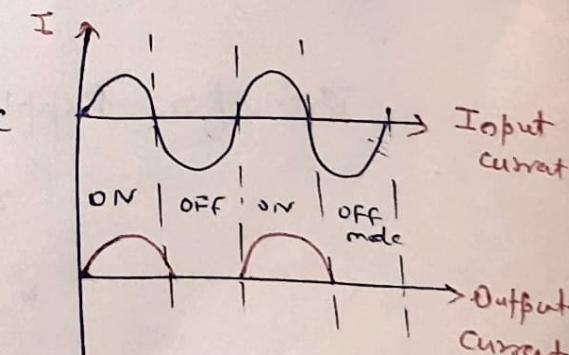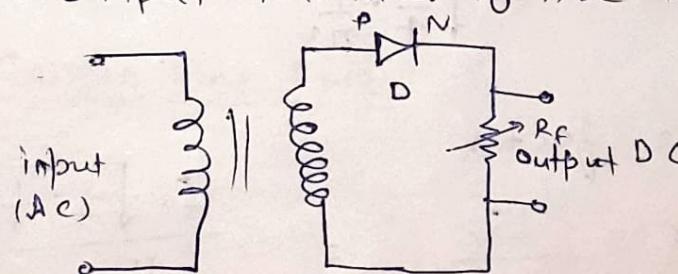1. Half wave Rectifier :-

Only positive half cycle of the AC voltage appears at the output terminal of the Rectifier.



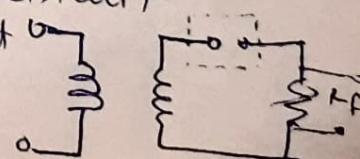In forward biased, Diode is in turn on mode
So current will show on output terminal as DC.
But in Reverse, it will work as open circuit
So no current will produce at output terminal.



Ripple factor :- The output wave of a rectifier is not a pure DC of constant magnitude.

It is an alternating wave with pulsation. These pulsations are called ripples.

[mixture of pure DC with pure AC component]

Ripple factor

$$\gamma = \frac{I_{AC}}{I_{DC}}$$

here
 $I_{DC} = I_{av}$
 ~~$I_{AC} = I_{rms}$~~

Output Power = power due to DC + power due to component AC component

$$I_{rms}^2 R_L = I_{DC}^2 R_L + I_{AC}^2 R_L$$

$$I_{rms} = \sqrt{I_{DC}^2 + I_{AC}^2}$$

$$I_{AC} = \sqrt{I_{rms}^2 - I_{DC}^2}$$

$$\therefore I_{DC} = I_{av} = \frac{2I_0}{\pi} \quad (\text{For half wave})$$

$$I_{rms} = I_0 \frac{\sqrt{2}}{2}$$

$$I_{AC} = \sqrt{\frac{I_0^2}{4} - \frac{I_0^2}{\pi^2}}$$

$$I_{AC} = I_0 \sqrt{\frac{1}{4} - \frac{1}{\pi^2}}$$

Therefore Ripple factor

$$\gamma = \frac{I_{AC}}{I_{DC}} = \frac{I_0 \sqrt{\frac{1}{4} - \frac{1}{\pi^2}}}{I_0 \frac{\sqrt{2}}{2}} = \frac{\sqrt{\frac{1}{4} - \frac{1}{\pi^2}}}{\frac{\sqrt{2}}{2}}$$

* $\boxed{\gamma = 1.21 \text{ or } 121\%}$

* Efficiency of Rectification:

$$\eta = \frac{\text{Output DC Power}}{\text{Input AC Power}}$$

$$\boxed{\eta = \frac{P_{DC}}{P_{AC}}}$$

$$\Rightarrow \eta = \frac{I_{AV}^2 R_L}{I_{rms}^2 (R_f + R_L)}$$


$$\left[\begin{array}{l} I_{AV} = \frac{I_0}{2\pi} \\ I_{rms} = I_m \sqrt{2} \end{array} \right]$$

$$\eta = \frac{\frac{I_0^2}{\pi^2} R_L}{\frac{I_m^2}{4} (R_L + R_f)}$$


$$\eta = 0.4053 \frac{1}{1 + R_f/R_L} \quad (R_L \gg R_f)$$

$$\eta = 0.40 \Rightarrow \% \eta = 40\% \text{ efficiency.}$$

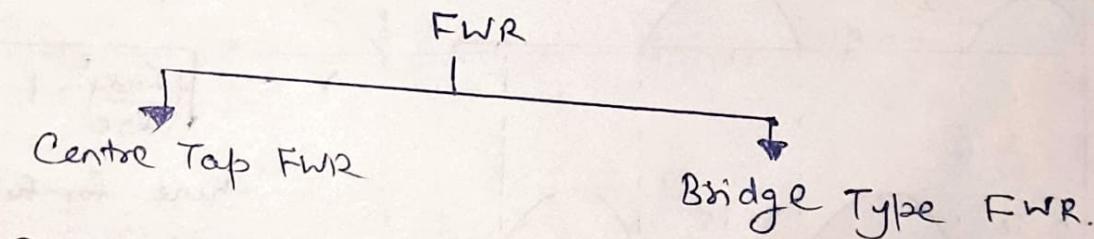(2) Full wave Rectifier:- It rectifies the full sinusoidal wave on AC current into DC.



(a) Centre Tap FWR

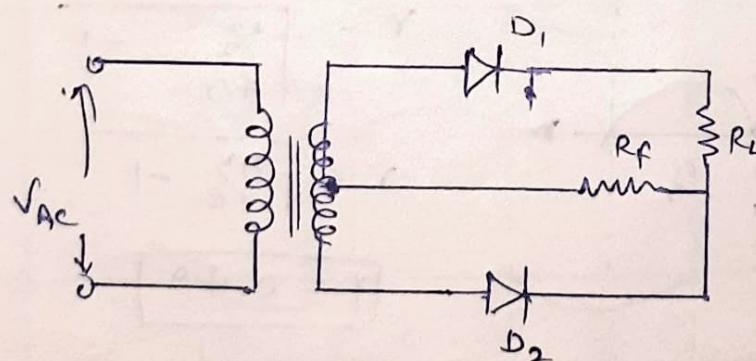


It consists two PN Diode & a centre tap transformer.


When we apply forward bias on the circuit, D₁ is activated & D₂ is in reverse biased so

only D₁ convert first (+)ive half current in DC.

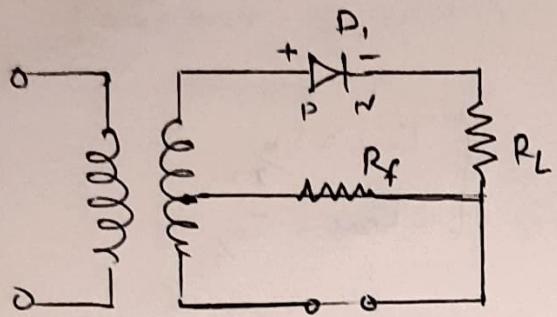
Similarly for D_2 ,
when reverse voltage applies on the circuit, D_2 is on active mode & converts the current current in DC.



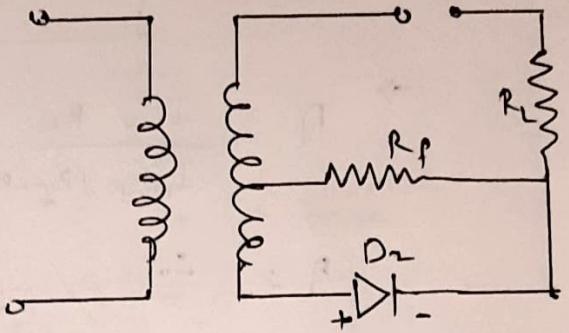D_1 is on turn on mode
 $\& D_2$ is on turn off mode
(Forward biased)



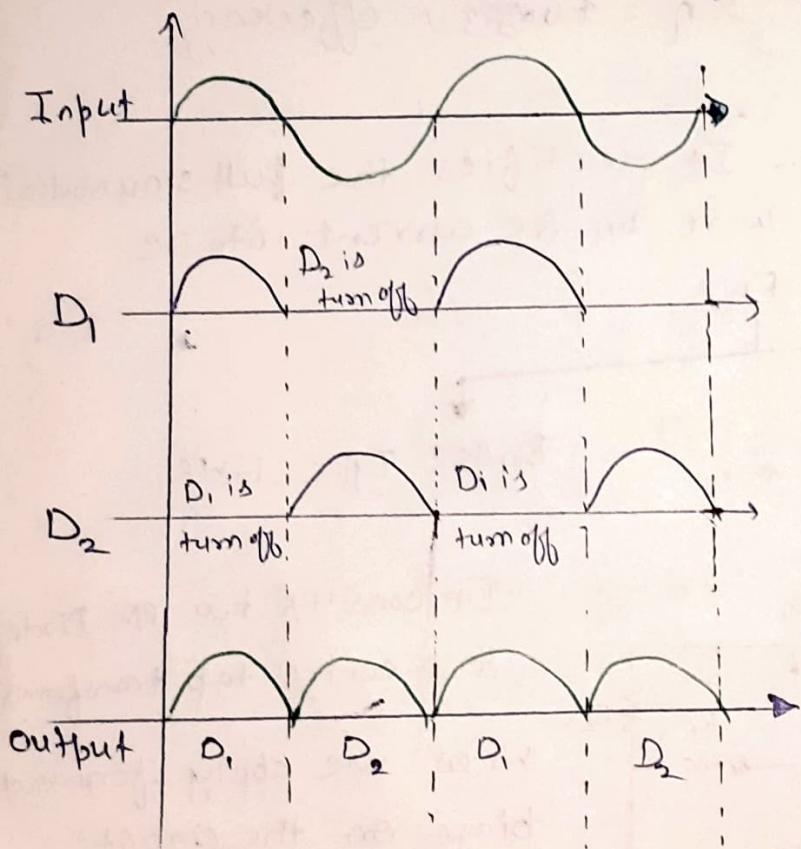D_2 is on turn on mode
 D_1 is on turn off mode
(Reverse biased)



$$V_o = \left[\frac{V_m \sin \theta}{R_L + R_f} \right] \times R_L$$

ripple factor

$$\gamma = \frac{I_{AC}}{I_{DC}} = \sqrt{\frac{I_{rms}^2 - I_{AV}^2}{I_{AV}^2}}$$

$$\gamma = \sqrt{\left(\frac{I_{rms}}{I_{AC}} \right)^2 - 1}$$

here for full wave

$$I_{rms} = I_{AV} \sqrt{2}, \quad I = \frac{2I_{AV}}{\pi}$$

$$\gamma = \sqrt{\frac{1}{4} - 1}$$

$$\gamma = \sqrt{\frac{\pi^2}{8} - 1}$$


$$\boxed{\gamma = 0.49}$$

Efficiency $\eta = 0.8105$
 $= 81\%$


(B) Bridge Type Rectifier:- Can be used for High voltage

→ efficiency high than

FWR

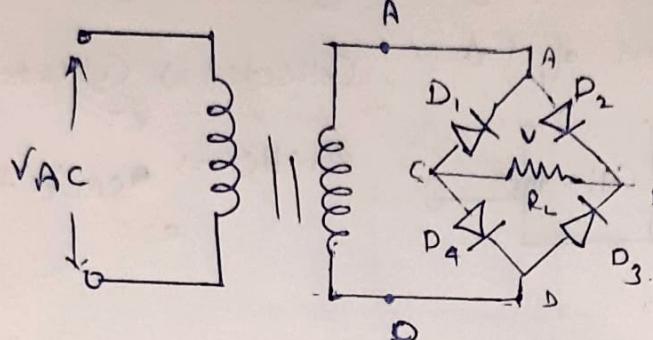


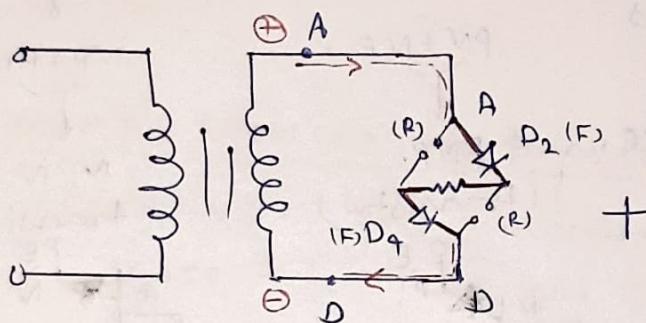when $A \rightarrow \oplus$
 $D \rightarrow \ominus$




D_1 & D_3 in turn off
& D_2 & D_4 in turn on.

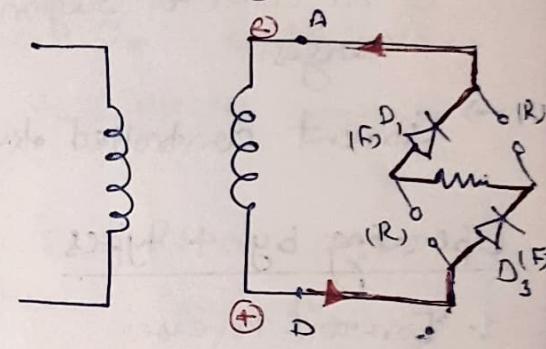when $A \rightarrow \ominus$
 $D \rightarrow \oplus$



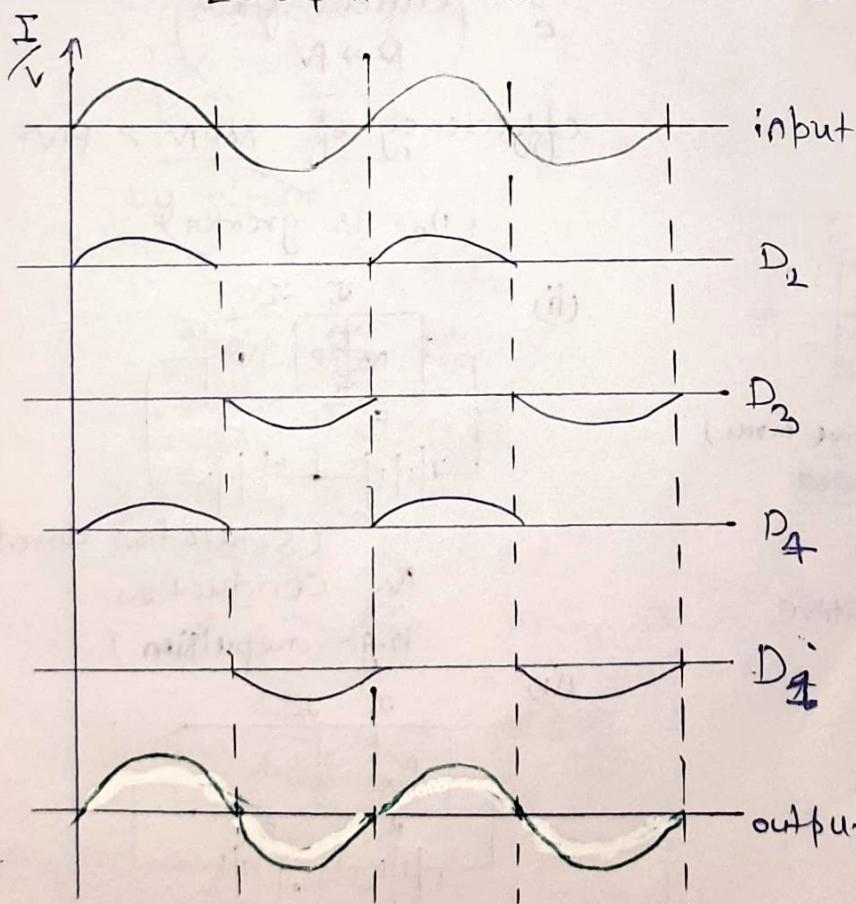D_1 , D_3 in turn on
& D_2 & D_4 in turn off.



$$V_o = \frac{V_m R_L \sin \theta}{(2R_f + R_L)}$$

* Frequency of Pulsation
 $\Rightarrow 2f$


* Transistor :- A semiconductor device, which have three terminals & generally made of Si or Ge.

(BJT)

It has 3 alternate layers of P & N.

→ Bipolar Junction Transistor.

(Amplifying the Signal)

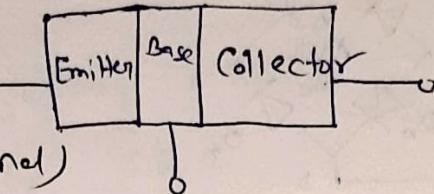

Collector \Rightarrow Collect the e-


Emitter \Rightarrow emit the e-

- Emitter is heavily doped
- Region of Base is smallest & for collector region is largest.

→ Current controlled device.


Operating by 4 types

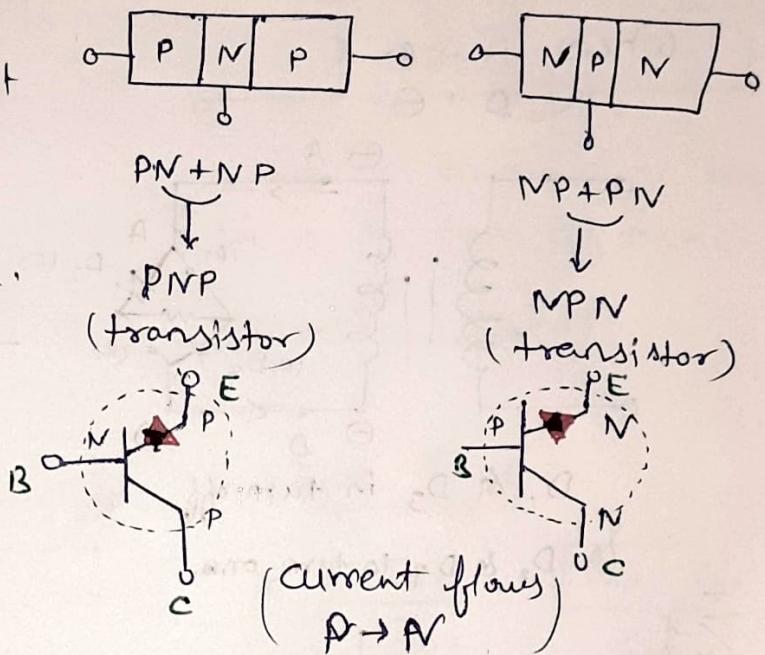1. Forward Reverse
2. Forward - Forward
3. Reverse - Reverse
4. Reverse - Forward.



efficiency of $NPN > PNP$


(n_e^- is greater)

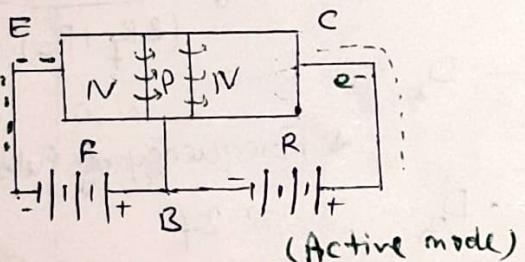

when E is in forward


bias, then the transistor will active

(ii)

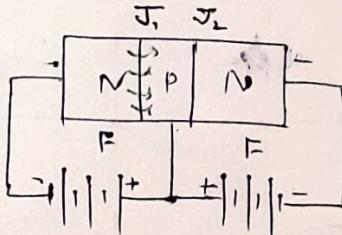


(Saturation current)
No conduction.
high repulsion.)

(iii)

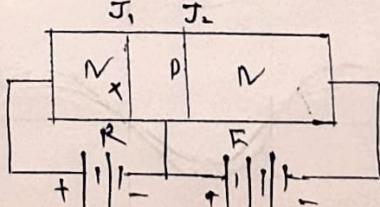



Junction 1. will break

(iv)

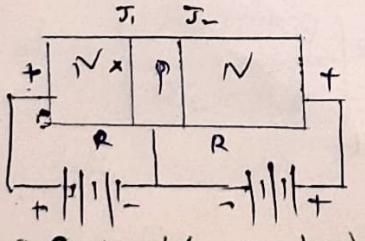

(Cut off mode)

Working of transistor:-

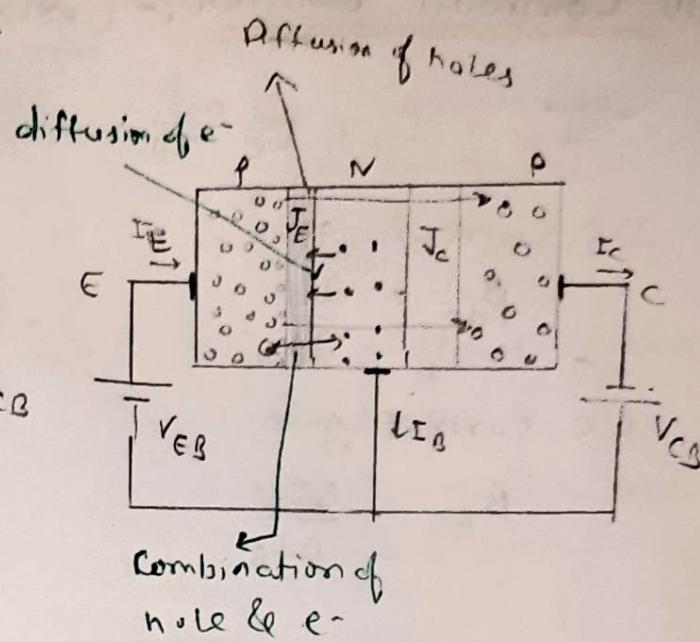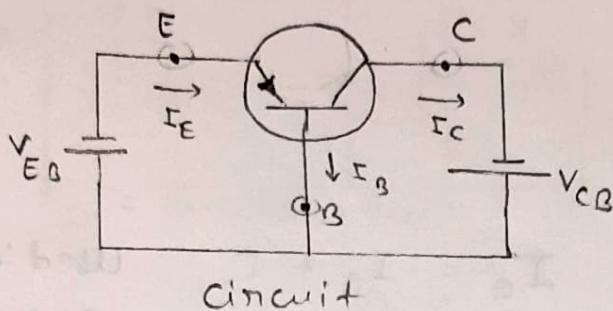

here J_E = Emitter Junction.

J_C = Collector Junction.

Common Connection of transistors

Transistor has 3 terminals & it is a 2 port device. So there are 3 type of connections -

1: Common base :-

→ DC current gain

$$\alpha_{dc} = \frac{I_C}{I_E}$$

by circuit

$$I_E = I_B + I_C$$


$$I_B = I_E - I_C$$

$$I_B = I_E - \alpha_{dc} I_E$$

Similarly for change in current

$$\Delta I_B = \Delta I_E - \alpha \Delta I_E \quad \alpha_{dc} \leftrightarrow \alpha_{AC}$$
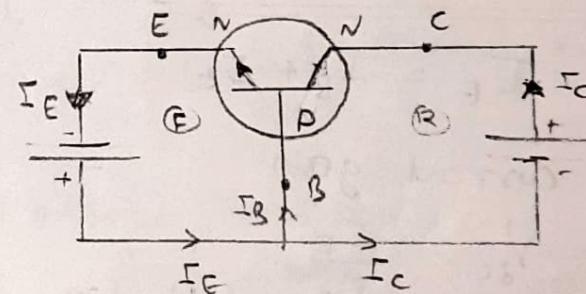
$$\frac{\Delta I_B}{\Delta I_E} = 1 - \alpha$$



$$\alpha_{AC} = \frac{\Delta I_C}{\Delta I_E}$$

used in

multistage amplifier
for high frequency application.

$$\alpha_{AC} = 1 - \frac{\Delta I_B}{\Delta I_E}$$

(less than unity)

(ii) Common Emitter :- Also known as Emitter follower.

$$I_E = I_B + I_C \rightarrow$$

DC current gain

$$\beta_{dc} = \frac{I_C}{I_B}$$

AC current gain

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B}$$

$$\alpha + \alpha \beta = \beta$$

$$\alpha = \beta(\alpha - 1)$$

$$\beta = \frac{\alpha}{\alpha - 1}$$

Output current

$$I_C = \beta(I_B) + ((1+\beta)I_{CO})$$

(iii) Common Collector :-

$$I_E = I_B + I_C$$

DC current gain

$$\gamma_{dc} = \frac{I_E}{I_B}$$

$$\gamma_{ac} = \frac{\Delta I_E}{\Delta I_B}$$


or

$$I_E = I_B + I_C$$

$$i = \frac{I_B}{I_E} + \frac{I_C}{I_E}$$

$$1 = \frac{1}{\gamma} + \alpha$$

$$\gamma = \frac{1}{1-\alpha}$$

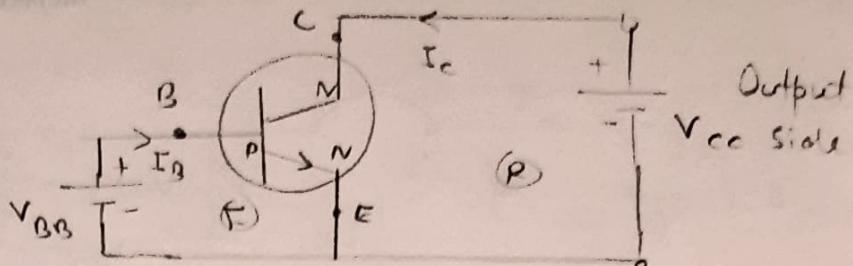


$$I_E = I_B + I_C$$

Used in
as an amplifier
specially in
audio
frequency.

$$\frac{I_E}{I_C} = \frac{I_B}{I_C} + 1$$

$$\frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\alpha = \frac{\beta}{1+\beta}$$

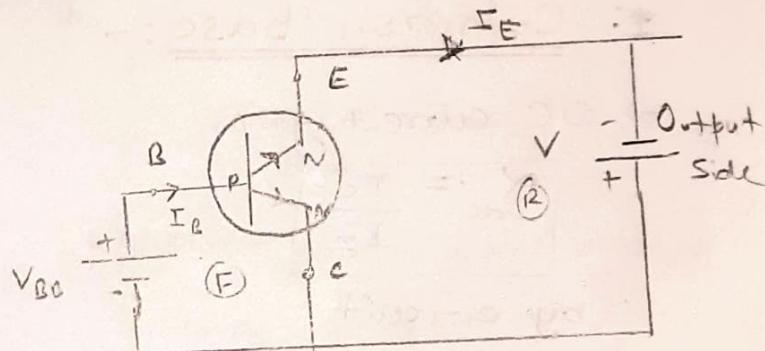

$$I_E = I_B + I_C$$

$$\frac{I_E}{I_B} = 1 + \frac{I_C}{I_B}$$

$$\gamma = 1 + \beta$$

Relation between γ & β

Output current


$$I_E = (\beta + 1)I_B + (1 + \beta)I_{CO}$$

due to minority
(charge carriers)

Relation Between γ & α

* FET (Field effect transistor)

→ It is a 3 terminal device

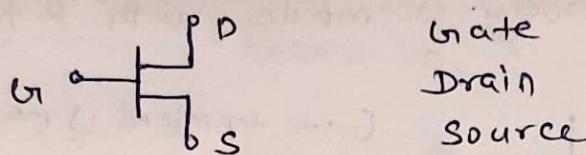



→ It is a voltage control device.

→ Unipolar device


→ Current flows in one direction.

→ Used for switch and, Amplifier.



FET

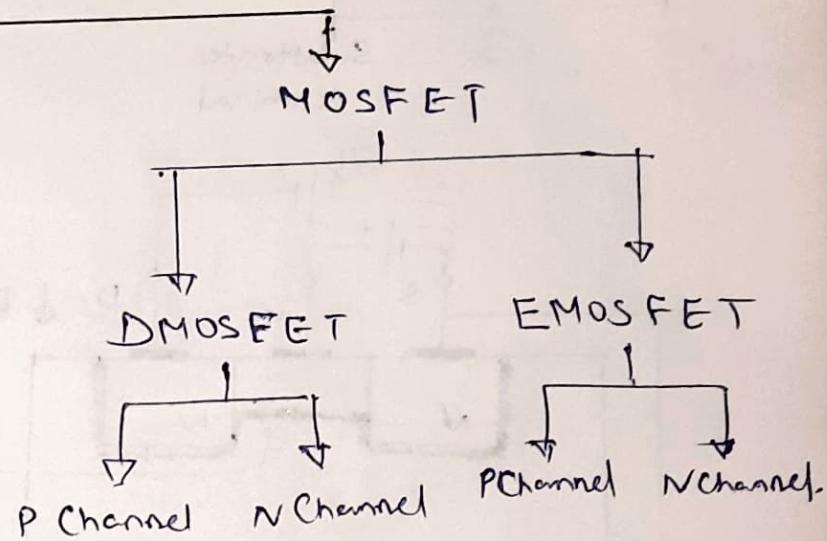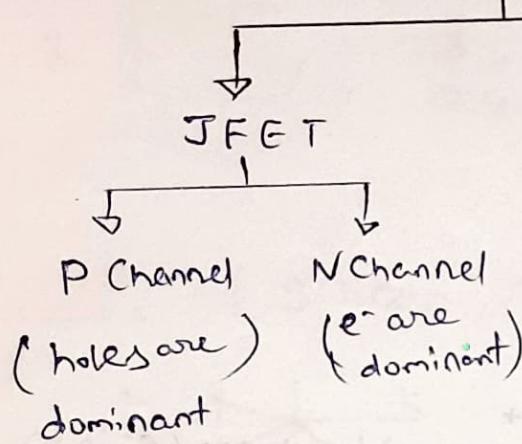

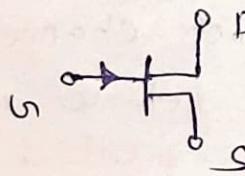(A) JFET :- (Junction Field effect Transistor)



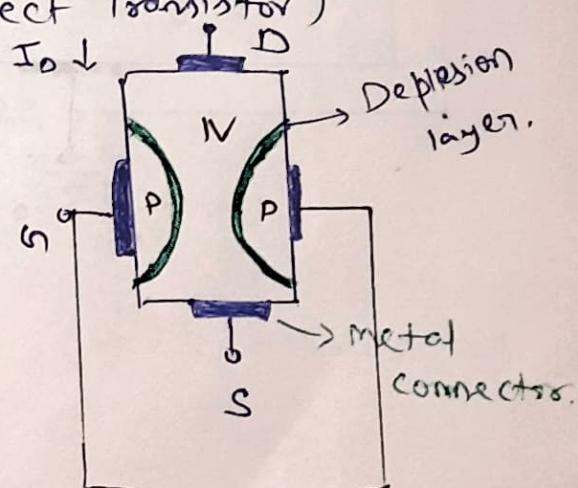
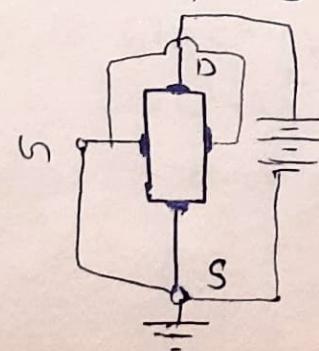
Battery is connect between D and S and $V_D < V_S \approx 0$



Both P are symmetric (Identical)
So they are connected.

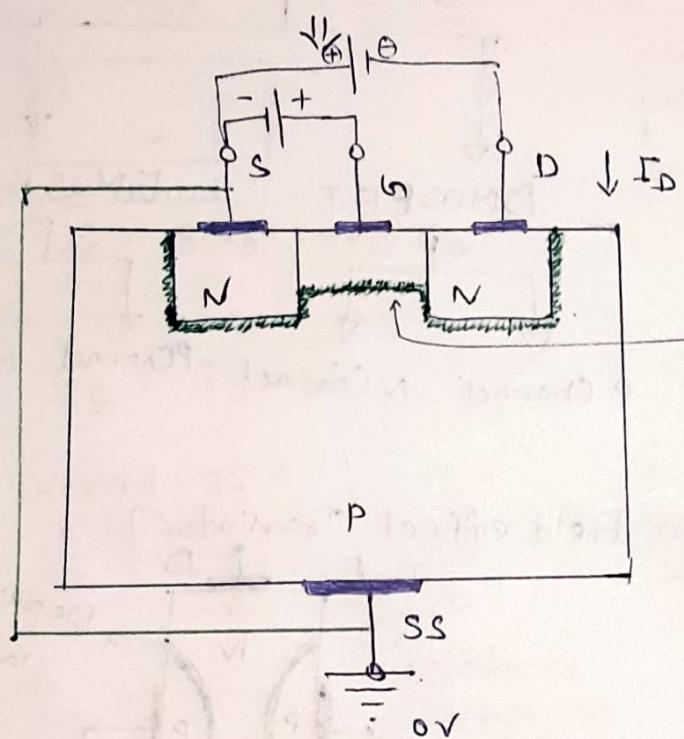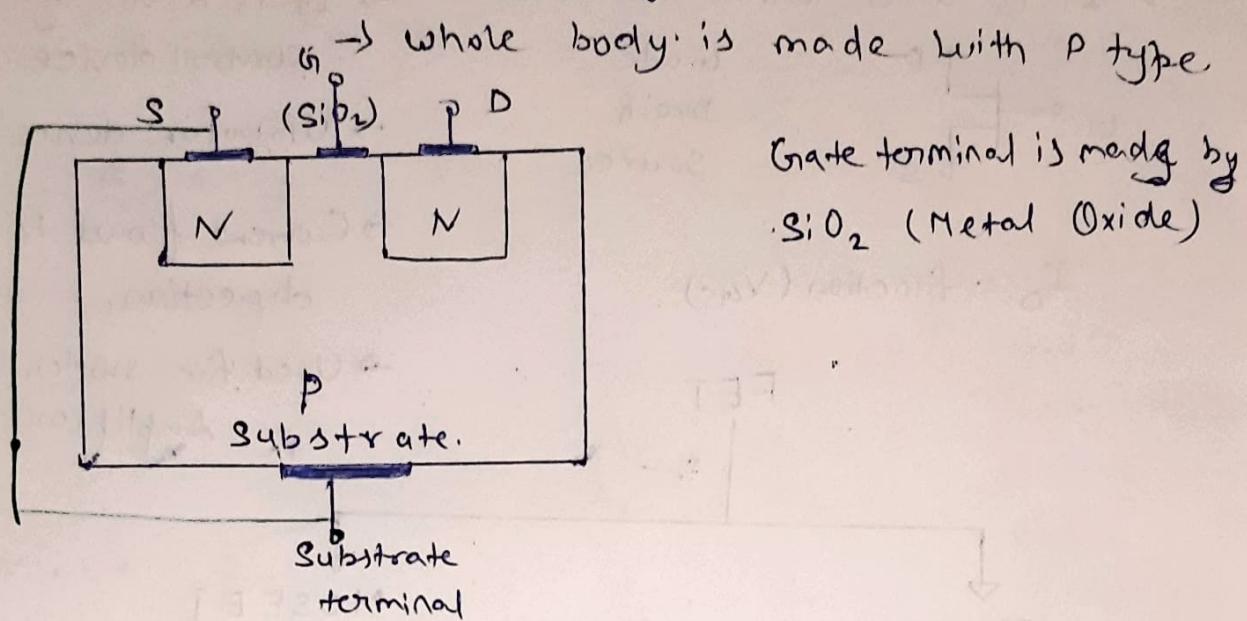(B) MOSFET

(Metal Oxide semiconductor Field effect transistor)





* Minority charge (e^- in P) will conduct current Between D to S

$V_{GS} =$ Threshold Potential
↳ at which channel create between N to N.

* IGBT :- (Insulated Gate bipolar transistor)


Used to a semiconductor device which is used in electronic switch.

→ Control by gate terminal.

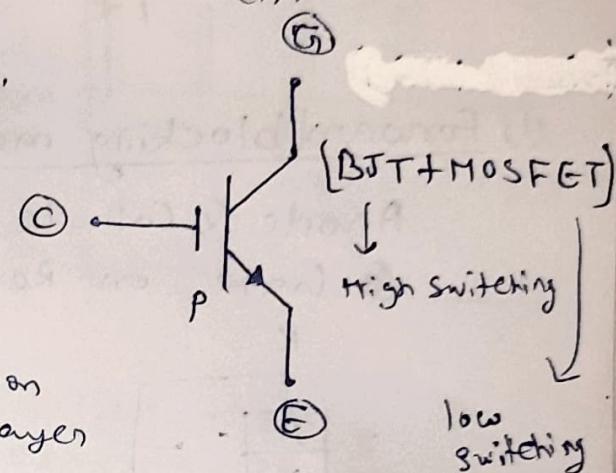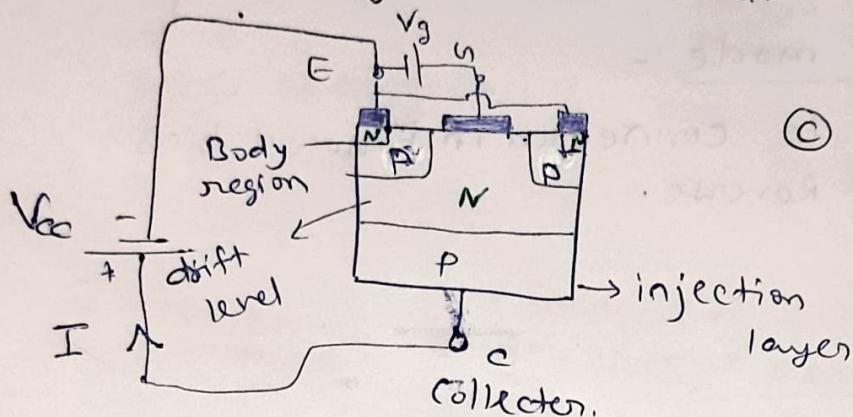

layer $\rightarrow \text{SiO}_2$

* SCR :- (Silicon Controlled Rectifier)

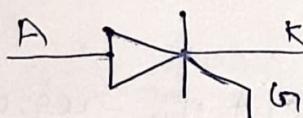


(Symbol)

Combo of P-N-P &
N-P-N transistor.

for some nano seconds
battery will be connected


or disconnected with
gate.

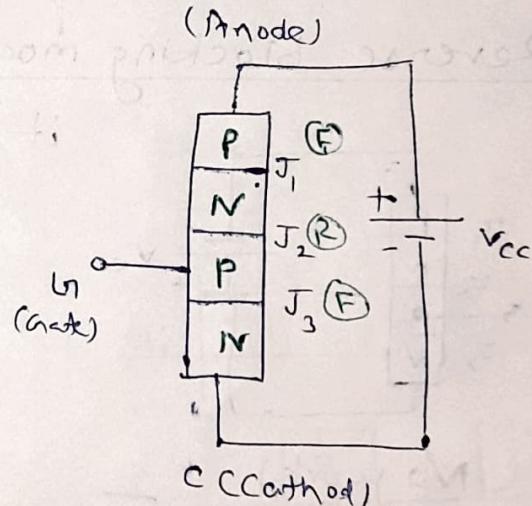- Forward blocking mode
- Reverse blocking mode
- Forward conducting mode.




Also known as

(Thyristor)

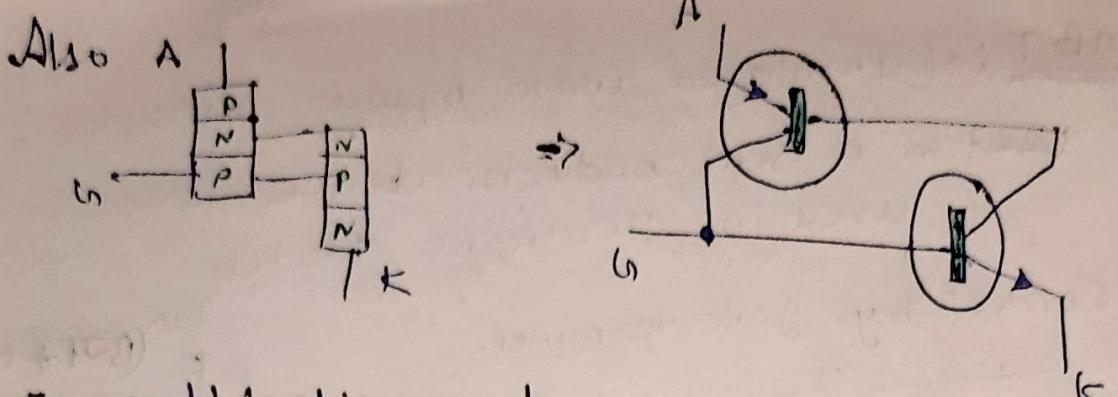

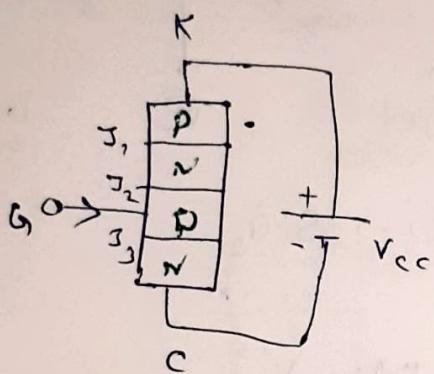(i) Forward blocking mode :-

Anode & Cathode connected in Forward bias.
& Gate on Reverse.



(ii) Reverse blocking mode :-


it is called cut off region mode

J₁ & J₃ \Rightarrow No conduction
(Reverse)

J₂ \Rightarrow Gate on forward biased.

(No work)


(iii) Forward Conduction mode :-

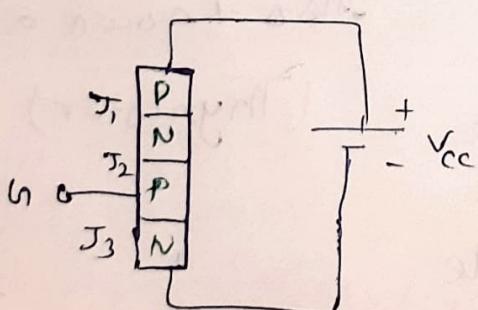

At a very high voltage at gate, Avalanche break is happens & J₂ junction will be on conduction mode

it is t Hence


J₁, J₂, J₃ \Rightarrow Conduction mode.

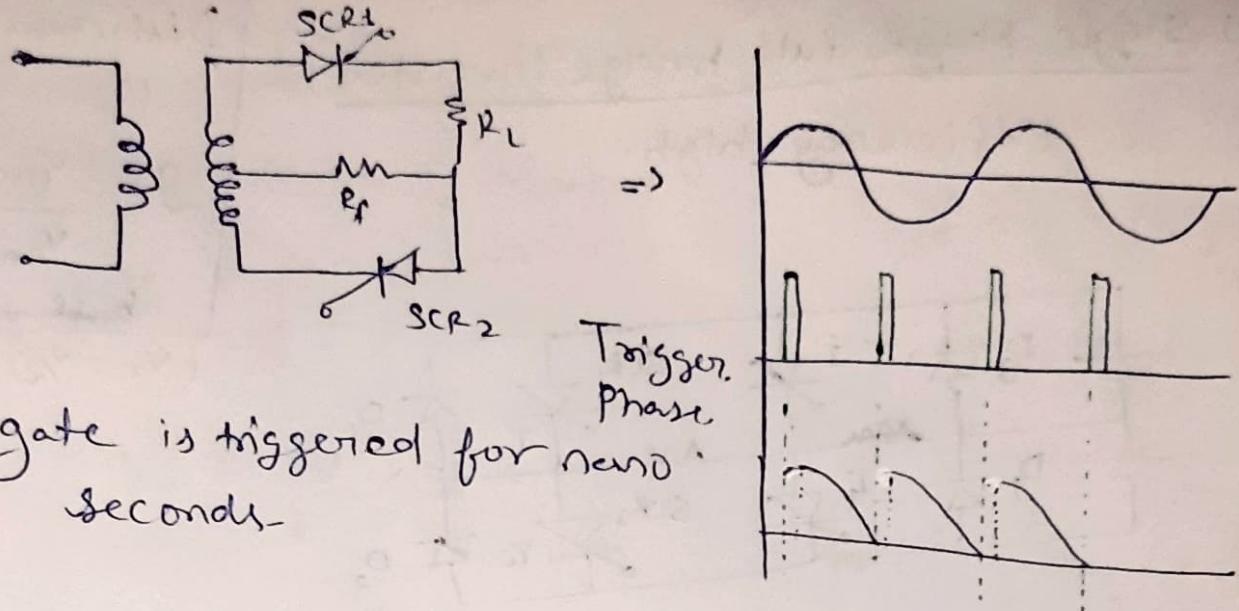

Inverter:- (fixed DC to variable AC)
A device that converts d.c power into
AC power at desired output voltage
& frequency. (Controlled device)
SCR \rightarrow at below $90^\circ \Rightarrow$ Rectifier
at above $90^\circ \Rightarrow$ inverter


* Single phase Bridge Inverter (DC \rightarrow AC)

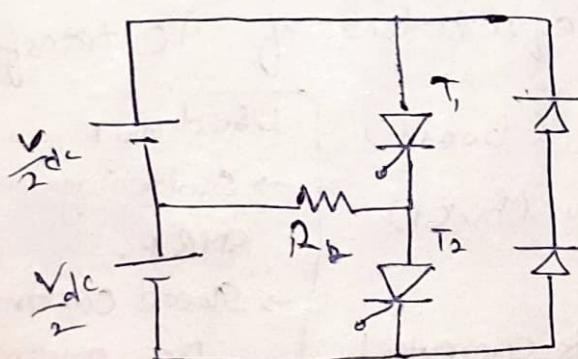(A) Single phase half bridge inverter:-
(Voltage Source)



Ig (1) gate pulse of SCR1


Ig (2) gate pulse of SCR2

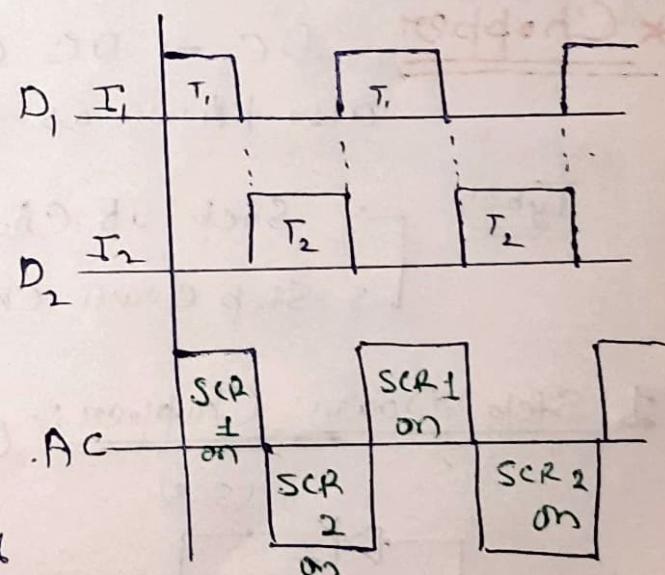

Rms value
 $V_{\text{rms}} = \frac{\sqrt{2} V_s}{\pi}$

(2) Single phase full bridge inverter:-

Efficiency, high.

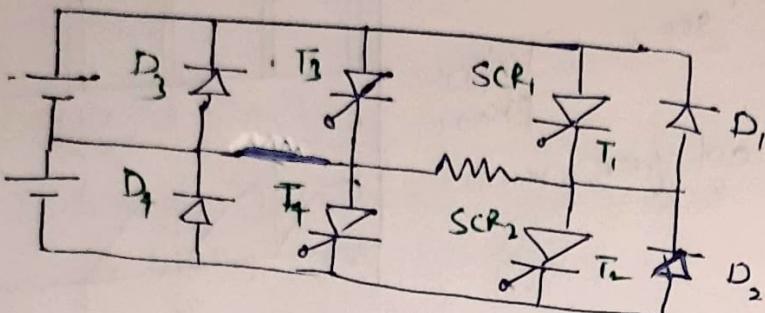


Distortion factor (3)

$$g = \frac{V_{rms}}{V_{rms}} = \frac{2\sqrt{2}}{\pi}$$

half wave

$$(V_o = V_{rms})$$

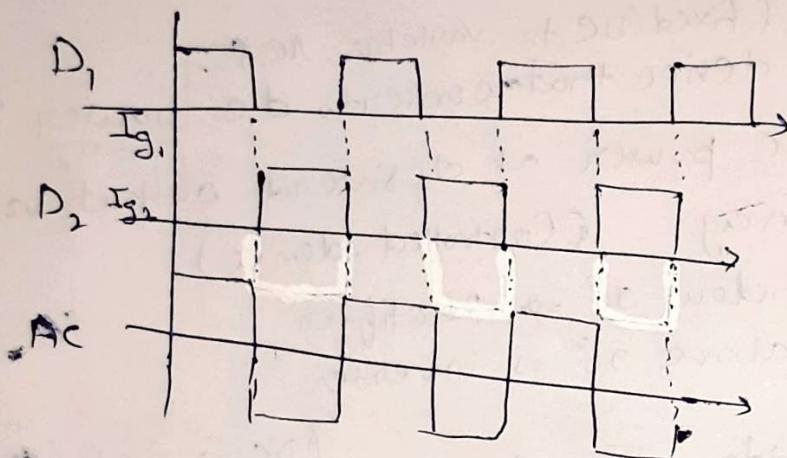

* Chopper


DC to DC converter (Controlled)

also known as DC equivalent of AC transformer

Types

- ↳ Step up Chopper (boost)
- ↳ Step down Chopper (buck)

1. Step Down Chopper:- (Buck converter)

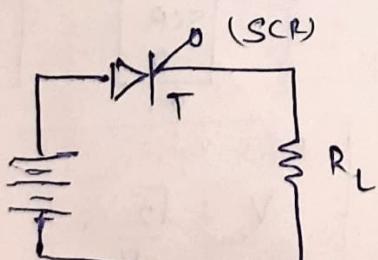

$$V_o = V \left(\frac{t_{on}}{t_{off} + t_{on}} \right)$$

V_{DC} = Avg value of output DC

I_{DC} = Avg current value of DC

It decrease Output DC voltage.

Used for

- Switching in PC, SMR P.
- Speed control in DC motor.

$$V_{DC} = V \left(\frac{d_{on}}{T} \right) = Vd$$

t_{on} = turn on time

t_{off} = turn off time.

RMS value of V output

$$V_o = \sqrt{\frac{1}{T} \int_0^{t_{on}} V^2 dt}$$

$$f = \frac{1}{T} \text{ (frequency)}$$

$$T = T_{on} + T_{off}$$


* d = duty cycle.

$$d = \frac{T_{on}}{T_{off} + T_{on}} = \frac{T_{on}}{T}$$

$$V_o = \sqrt{\frac{d_{on}}{T}} V$$

$$V_o = \sqrt{d} V$$

Step UP chopper (Boost converter)

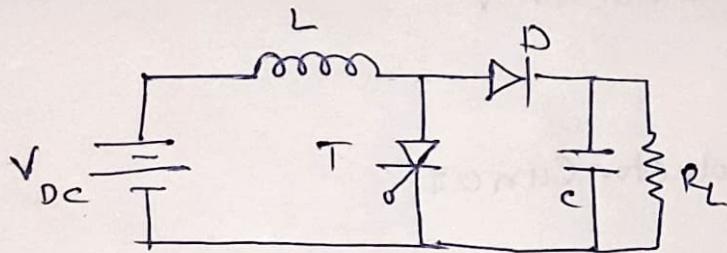

It Boosts output DC voltage.

$L \Rightarrow$ will store magnetic charge for T_{on} time.

C work as filter.

on turn off mode

L will release charge through D at load.

by KVL $V_{DC} = V_o + L \frac{di}{dt}$

Energy stored in inductor

$$E_L = V \cdot I \cdot d_{on}$$

$$\text{Voltage across } L = V_o - V$$

energy supplied by inductor

$$\text{at } t_{off} \Rightarrow L = (V - V_o) t_{off}$$

Energy stored inductor = Energy supplied by inductor.

$$VI_{\text{ton}} = (V_0 - V) I_{\text{off}}$$

(energy conservation)


$$V_0 = \frac{V [T_{\text{on}} + T_{\text{off}}]}{T_{\text{off}}} \quad (\because T_{\text{on}} + T_{\text{off}} = T)$$

$$V_0 = \frac{VT}{T - T_{\text{on}}}$$

$$V_0 = \frac{V}{1 - \frac{T_{\text{on}}}{T}} \quad (\because \frac{T_{\text{on}}}{T} = d)$$



$$\boxed{V_0 = \frac{V}{1-d}}$$

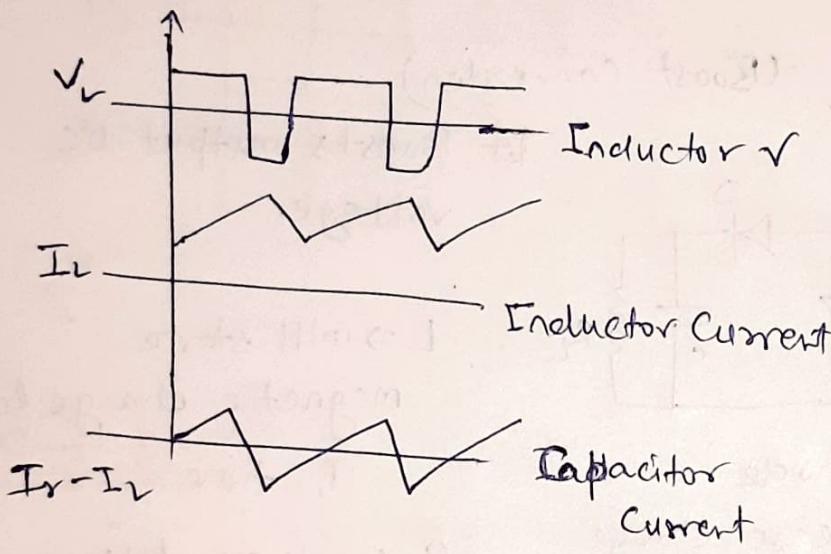


* Controlling Chopper

(i) PWM (Pulse width modulation)

(ii) Variable frequency

(iii) PWM

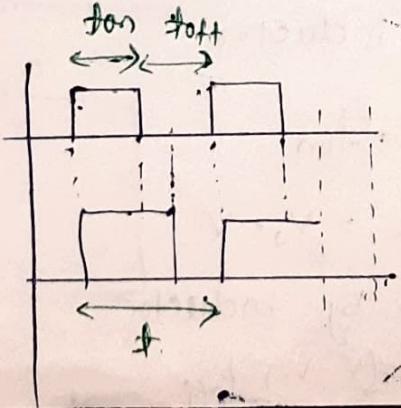

Total time = $t_{\text{on}} + t_{\text{off}}$

= Constant


No change in frequency.

(Changing in pulse)

$T_{\text{off}} \downarrow \& T_{\text{on}} \uparrow$

(ii) Variable frequency Control

(Costly)

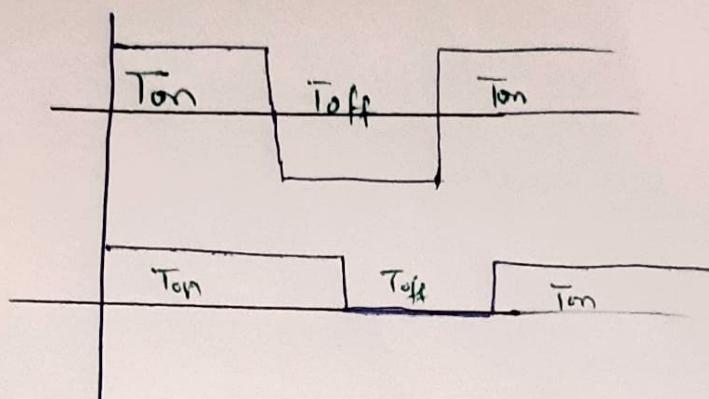

$T_{on} \uparrow$

$T_{off} \Rightarrow \text{constant}$

So f will change