

Electrical Installations

* Unit - 6 *

Switch Gear:- Used for electrical circuit switching, protection and controlling against overloads & short circuits.


• Classification - basis of voltage level -

- (1) Low voltage (LV) - up to 1 KV
- (2) medium voltage (MV) - 3 KV to 33 KV
- (3) High voltage (HV) - Above 33 KV

* Low voltage (LV) switch gears -

Switches, fuses, circuit breakers, off load electrical isolators etc. (Relay)

→ connected in series with circuit

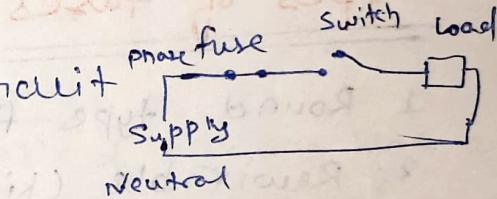

** Fuse

→ When an excessive current flows through the fuse then according to I^2Rt , heat is produced & fuse wire ^{will} melt so that circuit becomes open.

→ material for fuse wire

- Low melting point
- High conductivity
- Low cost
- Low ohmic loss

Ex: Zinc, Copper, tin etc

→ Advantage

- No need of maintenance
- breaks circuit without any noise or smoke
- cheapest form.

→ Disadvantage

If has to be replaced after each operation.

Switches

Metallogen. It consists of

A device which is used for opening or closing of electrical circuit.

Fuse

Short piece of wire which melt when excess current flow through it.


Circuit breaker:- To operate manually under normal condition & automatically under fault condition.

Relay:- To detect the fault & give the require info to the breakers for circuit is

• Types of fuses

- 1 Round type fuse unit
2. Rewirable (kit-kat) type fuse
3. Cartridge Type fuse

(1) Kit - kat type

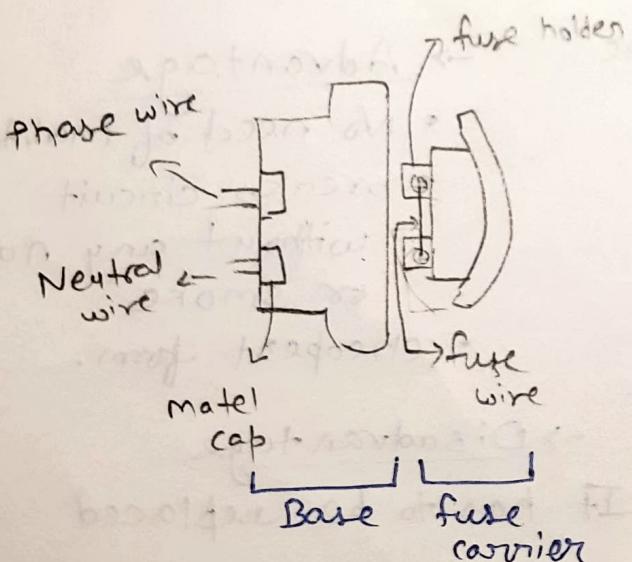

Rating upto 100 A

Advantage


- Easy to remove & replace
- fuse of negligible cost

Disadvantage

- Lack of discrimination
- Small time lag
- No current limiting

feature.

(2) Cartridge type fuse

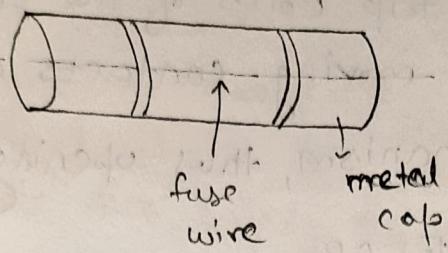

Advantage

→ Non spoilable fuse element for long time period due to insulation

→ Usually more accurate.

Disadvantage


→ More expensive to replace

→ Totally enclosed type fuse

→ Cartridge filled with
{ powder or granular material,
(filler) (Sand, CaCO_3 , quartz)

current rating upto 800A

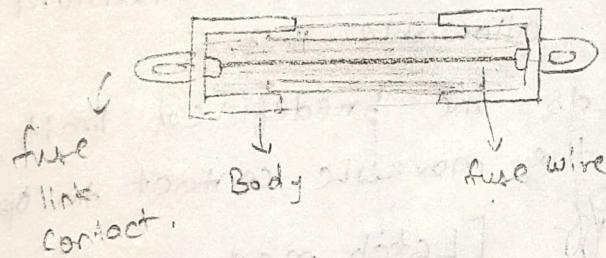(3) H.R.C. (High Rupturing Capacity) fuse -



Advantage

→ Capable of clearing high as well as low fault current

→ High speed of operations.

Disadvantage

→ Body of ceramic cylinder.

→ They have to be replaced

→ Used at industry level.


after each operation.

CB When a fault occurs in any part of the system, the trip coils of the breaker get energized & the moving contacts are pulled apart by some mechanism, thus opening the ckt.

→ MCB MCCB ELCB

• MCB :- (Miniature Circuit Breaker)

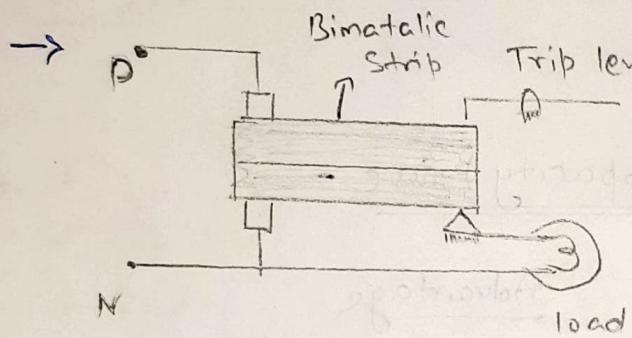Automatic operated switch under overload & in short circuit condition.



It is a switch which automatically turns off when the current flowing through it passes the maximum allowable limit.

When the current exceeds the predefined limit, a solenoid forces the movable contact to open. And the MCB turns off. [Latch mechanism]

Advantages

- (1) MCB's are replacing the re-wireable switch i.e., fuse units for low power domestic & industrial application.
- (2) MCB is combination of all three functions in a wiring system like → switching
→ Overload & short circuit protection.


Overload current → by bimetallic strip

Short circuit → Using solenoid

• ELCB

Earth leakage circuit Breaker.

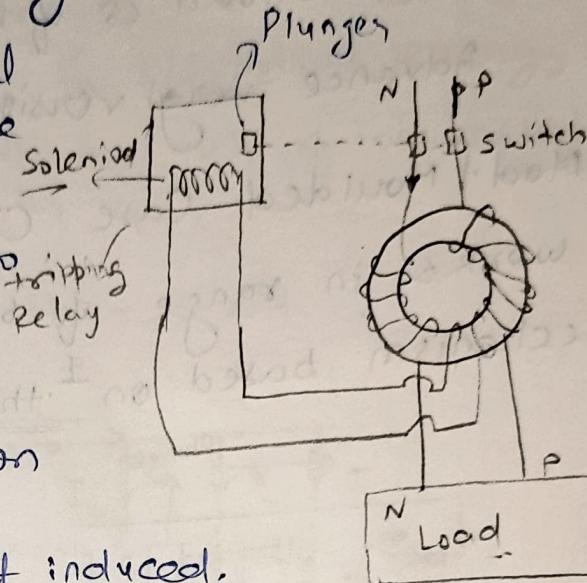- used with electrical machine to avoid the electrical shock & provide the safety to human or animal.



- In Normal condition

$$B_{net} = 0$$

So no current induced.

- In faulty condition

due Earth leakage


$$B_{net} \neq 0$$

So current will induce \rightarrow tripping relay
plunger will be pulled due
to induced magnetic field. &
break the circuit.

CELCB

* CGLCB \Rightarrow Current earth leakage circuit Breaker

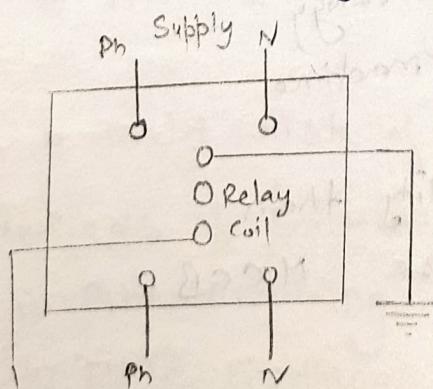* VELCB \Rightarrow Voltage earth leakage circuit Breaker.



Sense the sufficient voltage
and exceed voltage will
be grounded.

Connect to
metal body part.

VELCB


• MCCB Used to protect the circuit from overload & from short circuit condition.

Advance ~~verg~~ version of MCB.

Model: [Moulded Case Circuit Breaker]

→ Works in range of 63A to 3000A.

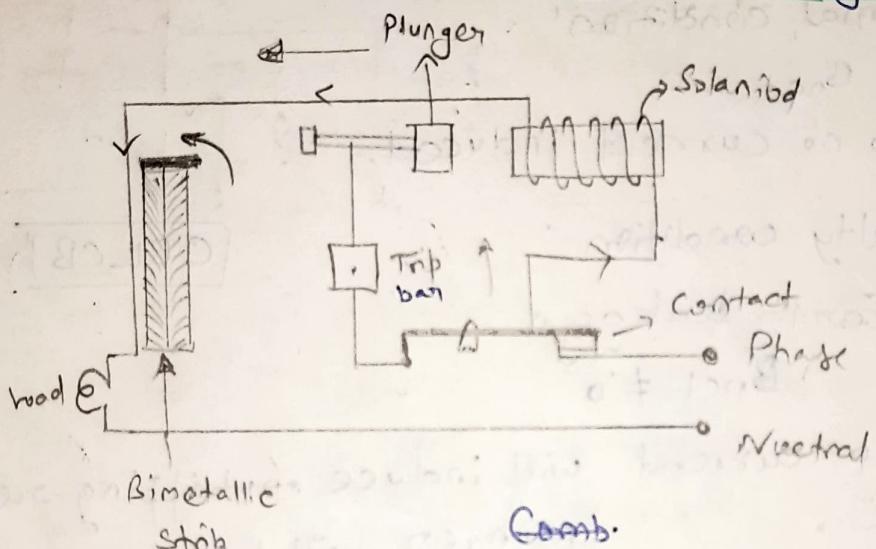* Mechanism based on thermal-magnetic circuit



If Strip take extra time to bend then Solenoid will take charge & strike the Trip bar. and open the circuit.

Advantage

Economical & tested technology


Advance high power machine

Disadvantage

Provide less flexibility than electronic release MCCB.

* Earthing :- The process of transferring immediate discharge of electrical energy directly to the earth with the help of low resistance wire.

* Potential of earth = 0 Volt

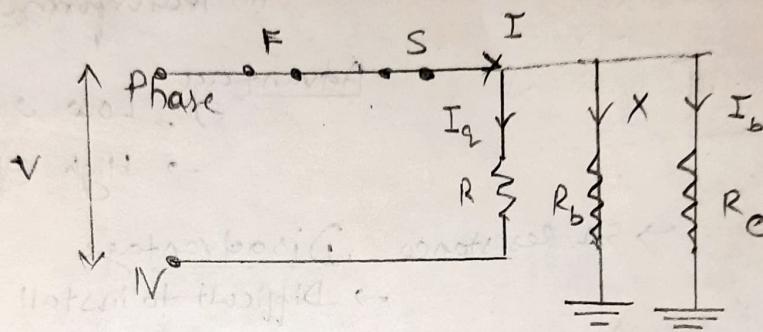

The earth resistance is affected by -

- Material properties of earth, wire & electrode.
- Temperature & moisture content of soil.
- Depth of pit.
- Quantity of charcoal.

o Necessity of Earthing :-

- To protect the operating personnel from shock.
- To maintain line voltage constant under unbalanced condition.
- To avoid risk of fire due to earth leakage current.


o Methods of Earthing :-

- Pipe Earthing
- Plate Earthing
- Rod earthing

- Strip or wire earthing

(1) Plate Earthing

Plate \rightarrow Galvanized Iron
or
Copper plate

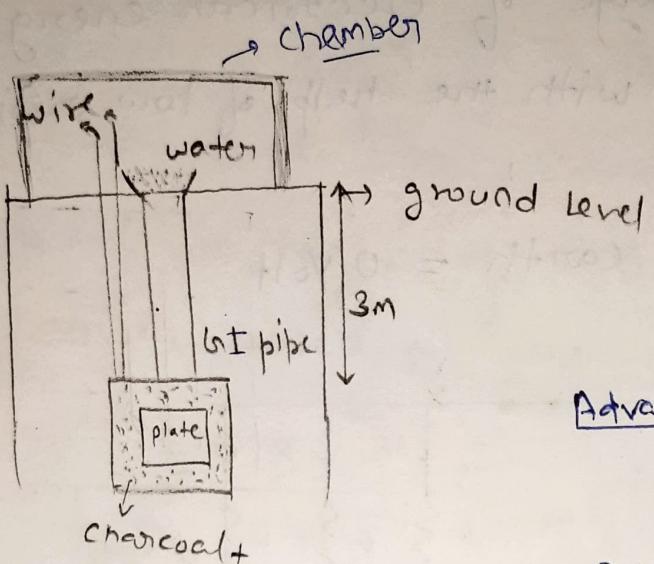

Application

- (i) Generator
- (ii) Transformer


Advantage \rightarrow Low resistance
 \rightarrow High Efficiency.

Disadvantage
 \rightarrow Difficult to install

(2) Pipe Earthing

diameter of 38 mm

length = 2m

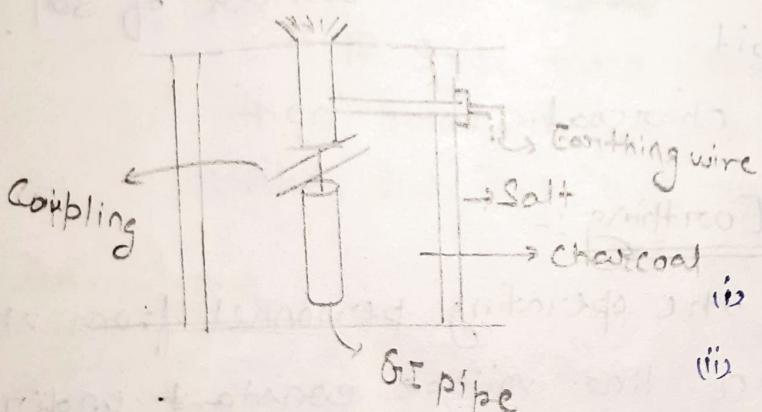

Application

- (i) Residential & Commercial


Advantage

- (i) Simple design
- (ii) Easy to install

Disadvantage

- (i) High impedance
- (ii) Hard to install in rocky salt.


(3) Rod Earthing

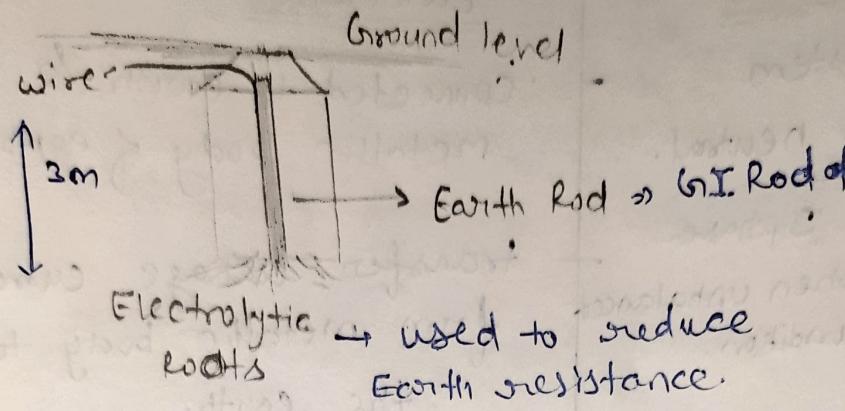

Application

→ Areas where soil is loose or sandy.

(4) Strip or Wire Earthing

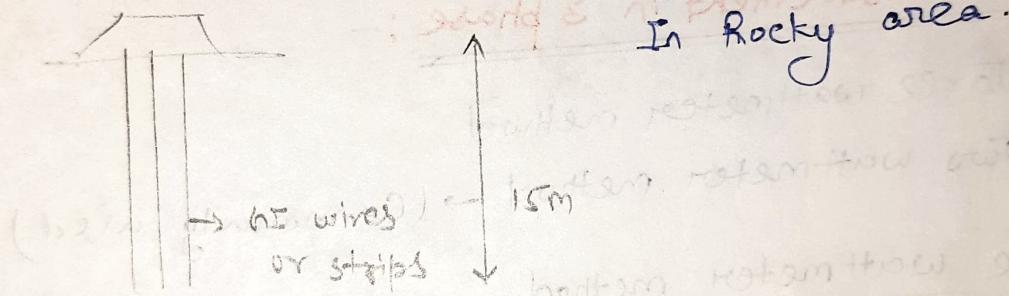

Application

In Rocky area.

Earth resistance → Should be kept as low as possible

It depends on

- Moisture, Condition or temperature of Soil.
- Depth of electrode, size, material of electrode.
- Quantity & quality of Soil + charcoal.


Difference between Earth wire & Neutral wire

<u>Neutral wire</u>	<u>Earth wire</u>
(i) In 3p - 4w system 4th one is neutral.	Connected to earth & metallic body of equipment
(ii) Return path of 3-phase current when unbalanced condition.	Transfer leakage current from metallic body to the earth.
(iii) In single phase, act as return path of line current	

Power measurement in 3 phase :-

- (i) Three wattmeter method
- (ii) Two wattmeter method → (Commonly used)

(I) Three wattmeter method

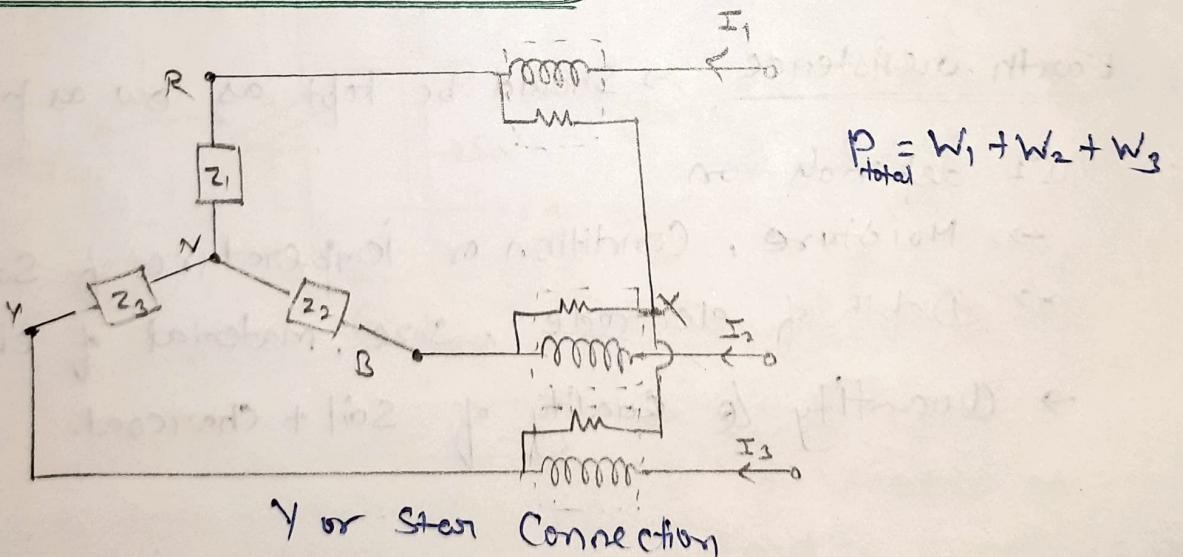

for Delta connection

X will neutral point.

Prove

Avg power by w_1 ,

$$w_1 = \frac{1}{T} \int_0^T V_{RN} i_1 dt$$

Similarly for w_2 & w_3

$$w_2 = \frac{1}{T} \int_0^T V_{YN} i_2 dt \quad w_3 = \frac{1}{T} \int_0^T V_{BN} i_3 dt$$

Total power

$$P = w_1 + w_2 + w_3$$

$$P = \frac{1}{T} \left[\int_0^T (V_{RN} i_1 + V_{YN} i_2 + V_{BN} i_3) dt \right]$$

$$\therefore V_{RN} = V_{RN} + V_{Nn}$$

$$\therefore I_1 + I_2 + I_3 = 0$$


$$\text{So } P = \frac{1}{T} \int_0^T (i_1 V_{RN} + V_{Nn} i_1 + V_{YN} i_2 + V_{BN} i_3 + \frac{V_{Nn}}{dt}) dt$$

$$P = \frac{1}{T} \int_0^T (V_{RN} i_1 + V_{YN} i_2 + V_{BN} i_3) dt = \text{Total power}$$

(2) Two-Wattmeter Method


Here, only two wattmeter will be connected.

$$w_1 + w_2 = \text{Total power}$$

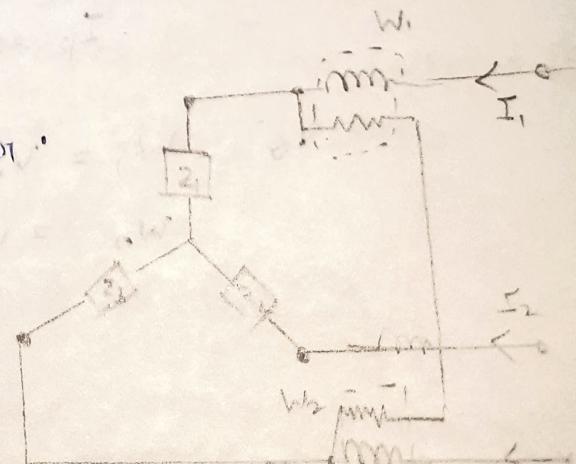

- It is useful to total power regardless of
- Load unbalance
 - Source unbalance
 - Difference in wattmeter
 - Wave-form of source
 - Phase sequence

Calculation of Power factor:-

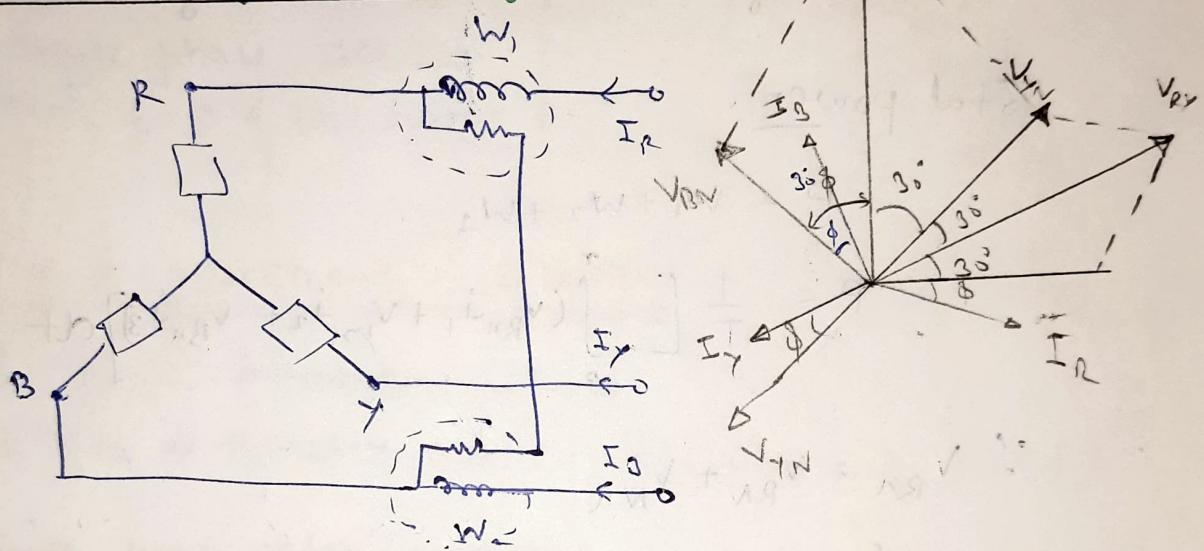

$$V_{RN} - V_{YN} = V_{RY}$$

$$W_1 = V_{RY} I_R \cos(30^\circ + \phi)$$

$$\text{Q} \quad W_2 = V_{BY} I_B \cos(30^\circ - \phi)$$

$$\therefore V_{RY} = V_{BY} \Rightarrow \text{line voltage} = V_L$$

$$I_R = I_B \Rightarrow \text{line current} = I_B$$

$$\text{So } W_1 = V_L I_L \cos(30^\circ + \phi)$$

$$W_2 = V_L I_L \cos(30^\circ - \phi)$$

$$P_{\text{Total}} = W_1 + W_2$$

$$P_T = V_L I_L (\cos(30^\circ + \phi) - \cos(30^\circ - \phi))$$

$$P_T = V_L I_L (2 \cos 30^\circ \cos \phi)$$

$$P_T = \sqrt{3} V_L I_L \cos \phi$$

* Power factor $\Rightarrow \frac{W_2 - W_1}{W_2 + W_1} = \sqrt{3} I_L \sin \phi$


$$\phi = \tan^{-1} \left(\sqrt{3} \frac{(W_2 - W_1)}{(W_2 + W_1)} \right)$$

Reactive Power $= \sqrt{3} (W_2 - W_1)$

Note

If The 3 phase load is balanced, then one wattmeter method is sufficient to measure power.

$$P_T = 3 \times W$$

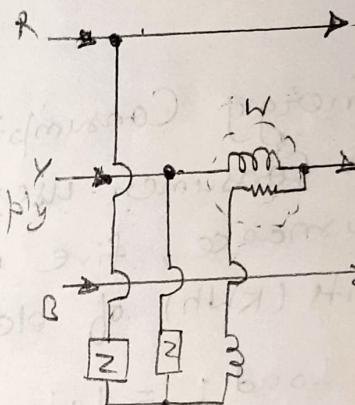

Example The power input to a 2000 v ; 50Hz , 3 phase motor running on full load at an efficiency of 90% , is measured by two wattmeters which indicate 300 kW & 100 kW respectively. Find (i) the input (ii) the inf power factor (iii) the line current & output ?

(i) Input $= W_1 + W_2 = 400 \text{ kW}$

$W_2 = 300 \text{ kW}$

(ii) power factor

$W_1 = 100 \text{ kW}$

$$\tan \phi = \sqrt{3} \left(\frac{W_2 - W_1}{W_2 + W_1} \right)$$

$$\phi = \tan^{-1} \left(\sqrt{3} \frac{1}{2} \right) = 40.9^\circ$$

$$\boxed{\phi = 40.9^\circ}$$

power factor = $\cos\phi$

$$= \cos(40^\circ)$$

$$= 0.756 \text{ Ans}$$

(iii) Output = input $\times 90\%$, = input $\times 0.9$

$$= 400 \times 0.9 = 360 \text{ kW}$$

Line current $I_L = ?$

$$W_T = \sqrt{3} V_L I_L \cos\phi$$

$$I_L = \frac{W_T}{\sqrt{3} V_L \cos\phi}$$

$$I_L = \frac{400 \times 10^3}{\sqrt{3} \times 2000 \times 0.756}$$

$$\boxed{I_L = 152.74 \text{ A}} \quad \underline{\text{Answer}}$$

Q Energy Consumption -

$$\boxed{1 \text{ unit} = 1 \text{ kWh}}$$

A Consumer uses a 10kw geear, a 6kw electrical furnace, five 100w bulbs for 15 hours. How many units (kWh) of electrical energy have been used?

Soln Load 1 = 10 kw geear

Load 2 = 6 kw electrical furnace

Load 3 = 500 watt (5 \times 100 watt bulbs) = 0.5 kW

Total Load = 16.5 kW

Total time taken = 15 hrs

Energy Consumed = 15×16.5 (Power \times time)
 $= 247.5 \text{ kWh}$

Then total energy consumption (in units)

$$= 247.5 \text{ unit}$$